


RF Power Amplifier Design Considerations for Amateur Radio



Zack Costello | CostelloZD@cardiff.ac.uk | 16th March 2019

Introduction

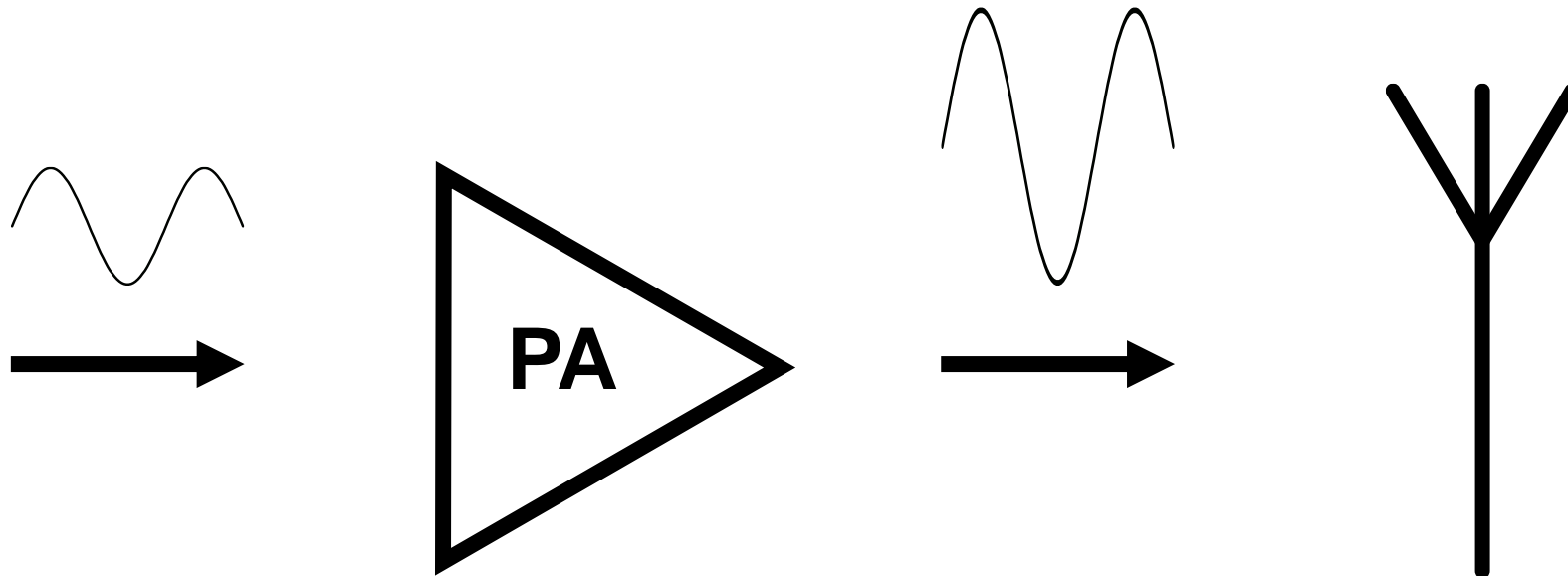Why are RF power amplifiers (PAs) important for amateur radio?



Generate the transmitted power used in transmission –
Cannot operate without them!

Commercial CAD Tools

Most popular industry electronic design automation (EDA) tools:

- Keysight Advanced Design System (ADS)
- AWR Microwave Office (MWO)

Very powerful tools BUT they are also very expensive, particularly for an individual user

Free CAD Tools

Looked for software that was free (and ideally open-source):

- What tools are needed for useful PA design software?
- What is currently available?
- What can they do?
- How does it compare against commercial software?

Talk Aim(s)

Demonstrate some PA design fundamentals
using free CAD tools

Will upload files to Cardiff ARS website: <https://www.cardiffars.org.uk/>

Begin building a learning toolkit similar to those on industry CAD packages
to gain greater understanding – But available to all!

Software Used


- *Quite Universal Circuit Simulator (Qucs)* – Circuit simulator
Several forks...

Qucs	Open Source	Linux, MacOS and Windows
Qucs-S	Open Source	Linux and Windows
QucsStudio	Closed Source 🚫	Windows only 🚫


Can pick and choose tools from each fork

- *SimSmith* – Smith chart tool
- *GNU Octave* – Free alternative to MATLAB

FET Transistor

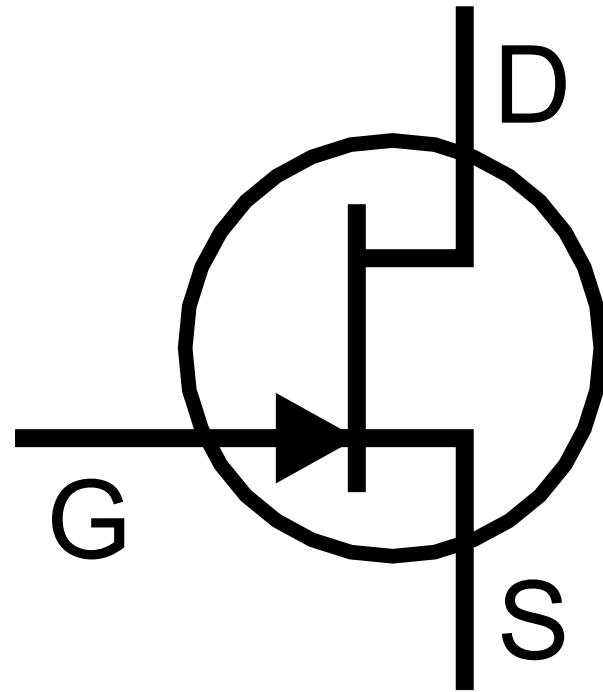


Current Generator Plane

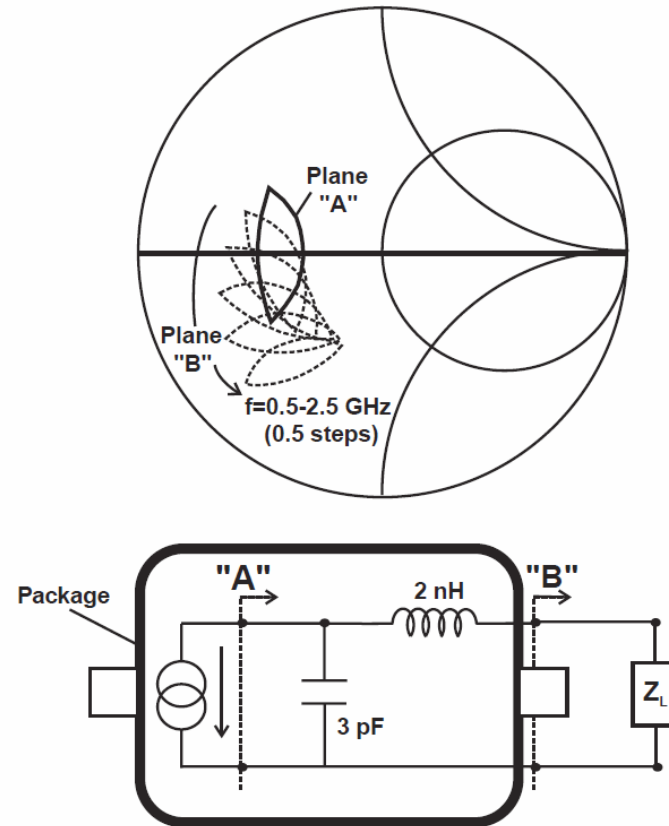


Cripps, S., 2006. *RF Power Amplifiers for Wireless Communications*. 2nd Ed. Artech House Inc., p. 30.

DC-IV Characteristic

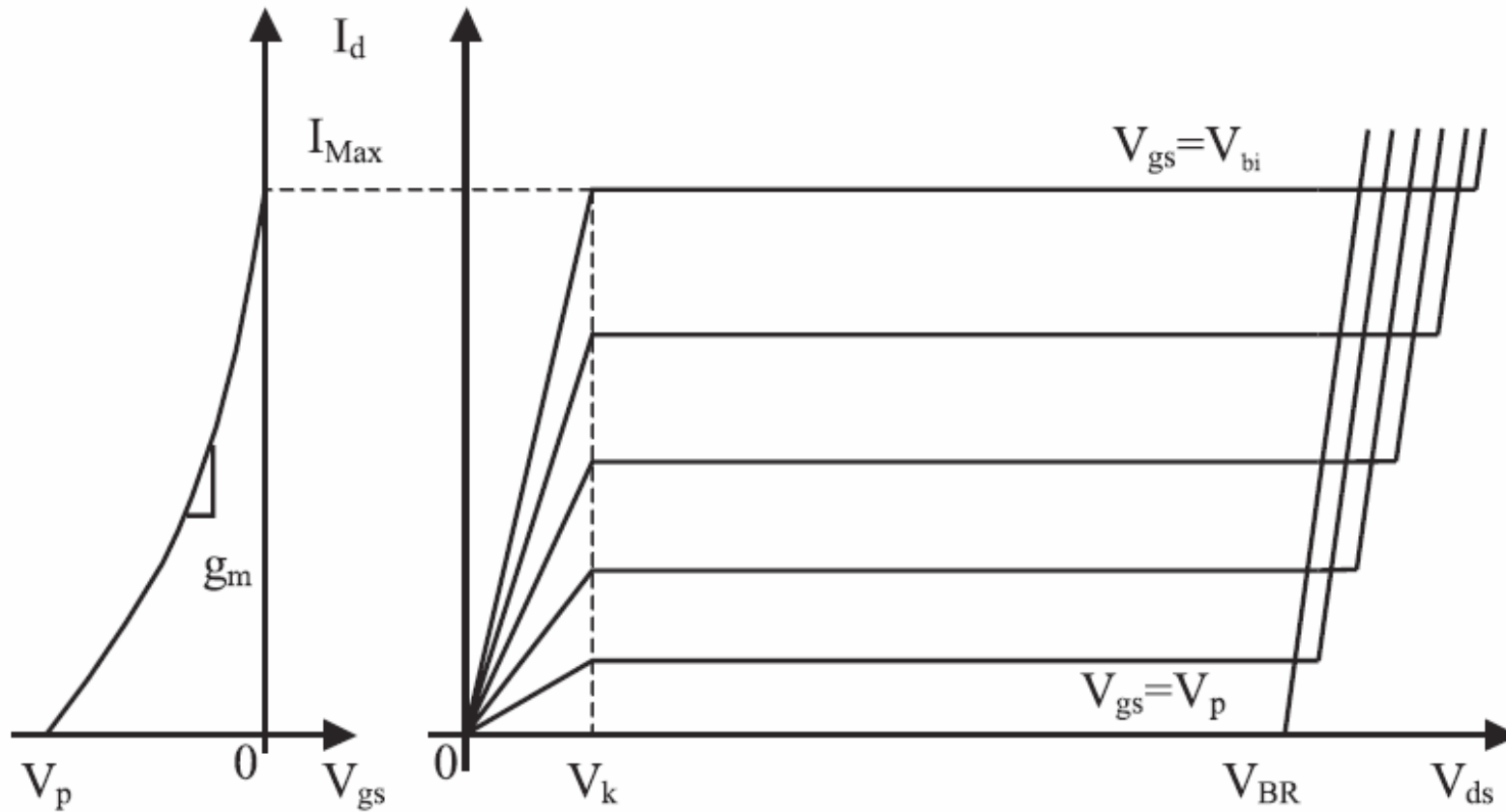


DC-IV Characteristic

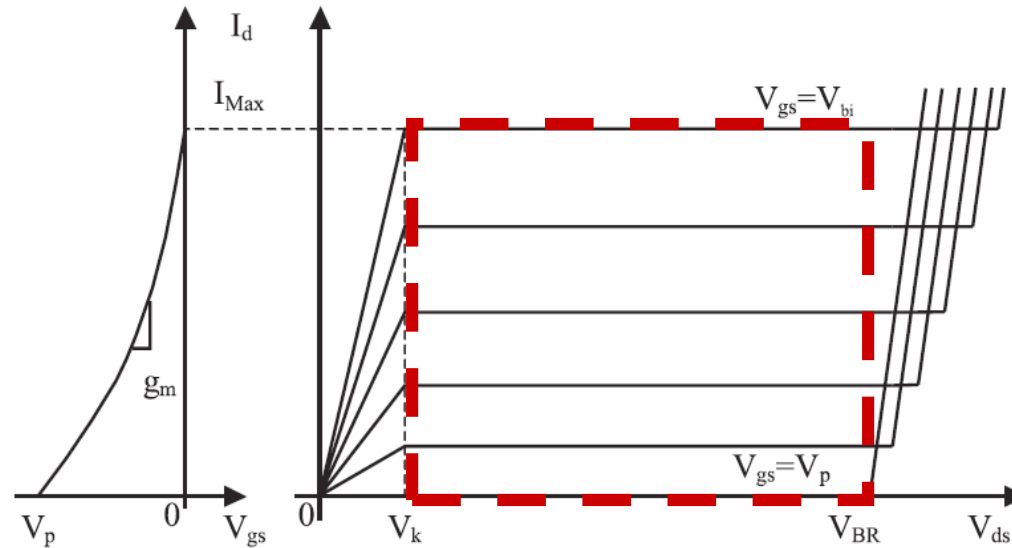


Apply a DC voltage to the drain-source (V_{DS}): The current will rapidly rise to a value at which it will remain for any further increase in drain voltage – *The saturation region*

DC-IV Characteristic

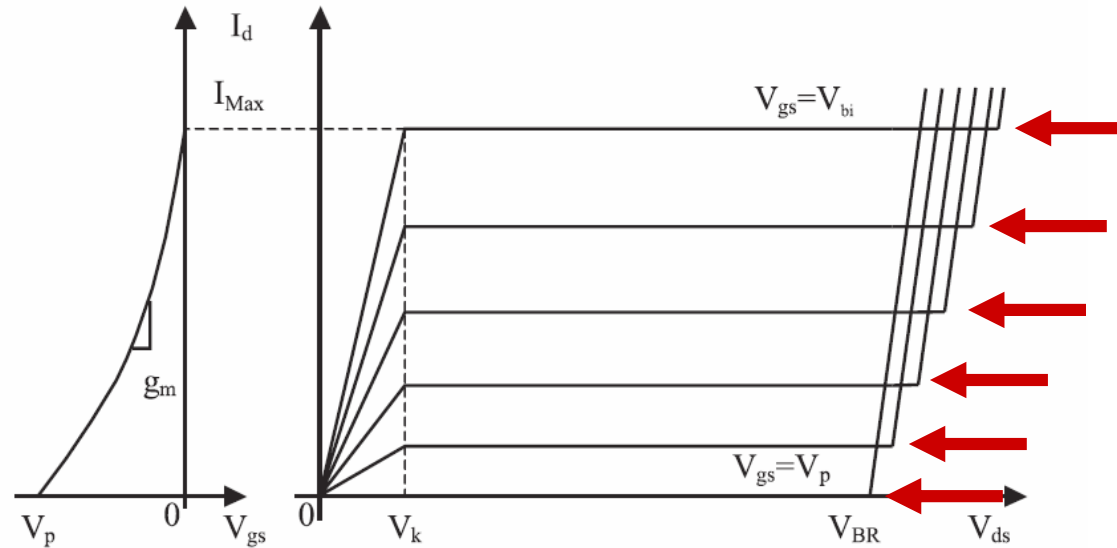


That saturated value is controlled by the DC voltage applied to the gate (V_{GS})

DC-IV Characteristic

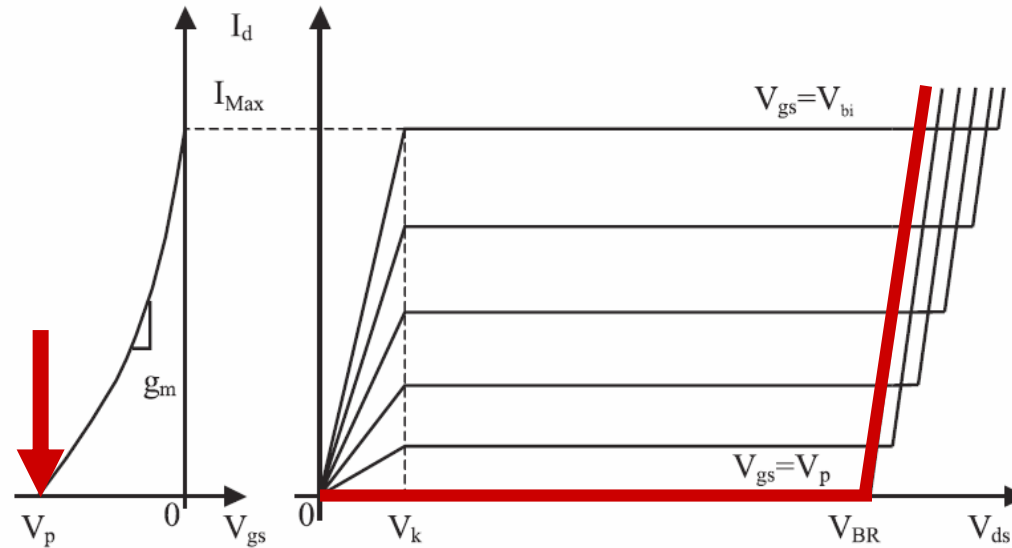

As you reduce the voltage on the gate there will come a point where there is (simply) no more current being drawn – The ‘**pinch-off**’ (or cut-off) voltage, V_p

DC-IV Characteristic

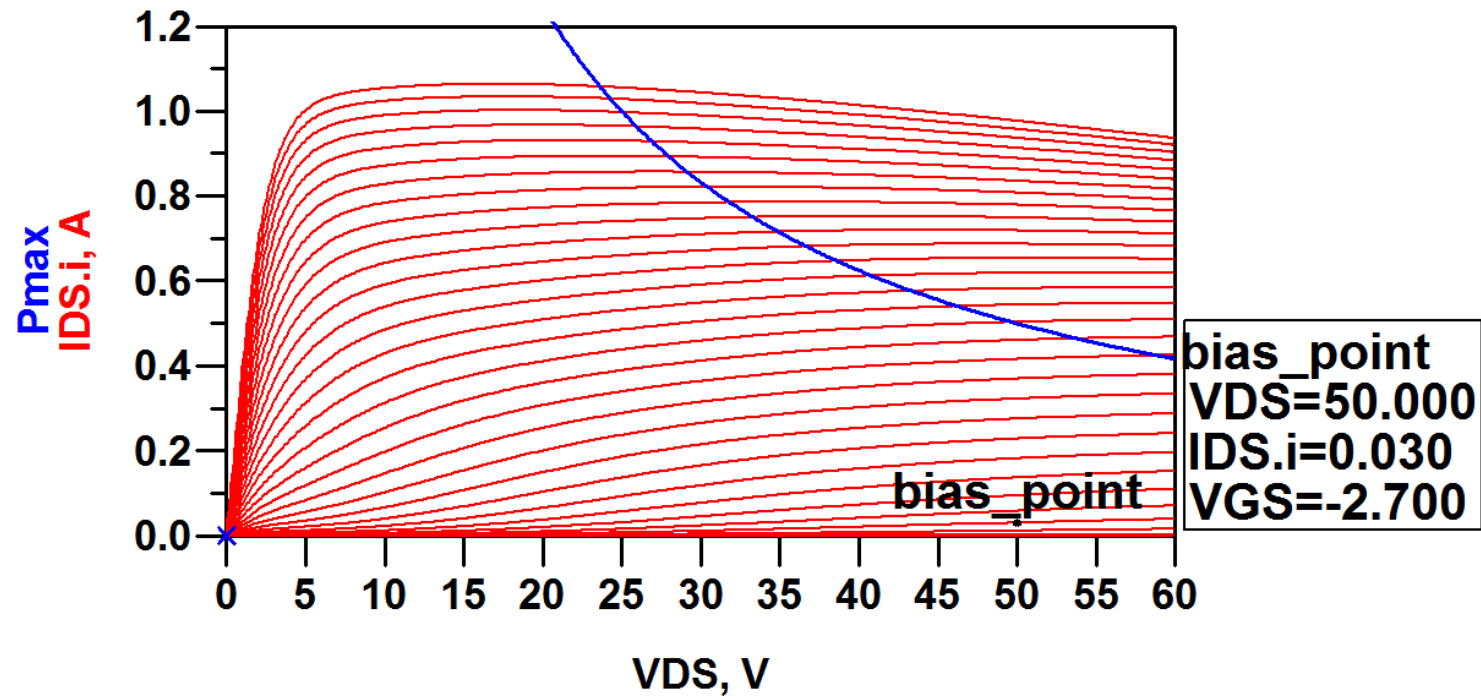

DC-IV Characteristic for Qorvo QPD1010 10W GaN Device


Load Line

- To create an output voltage a resistor is needed to complete the circuit: R_{opt} :


$$R_{OPT} = \frac{V_{RF}}{I_{RF}} = \frac{V_{DC}}{I_{MAX}/2}$$

- This will allow us to extract the maximum power from a given transistor


Biasing: 'Classic' Amplifier Classes

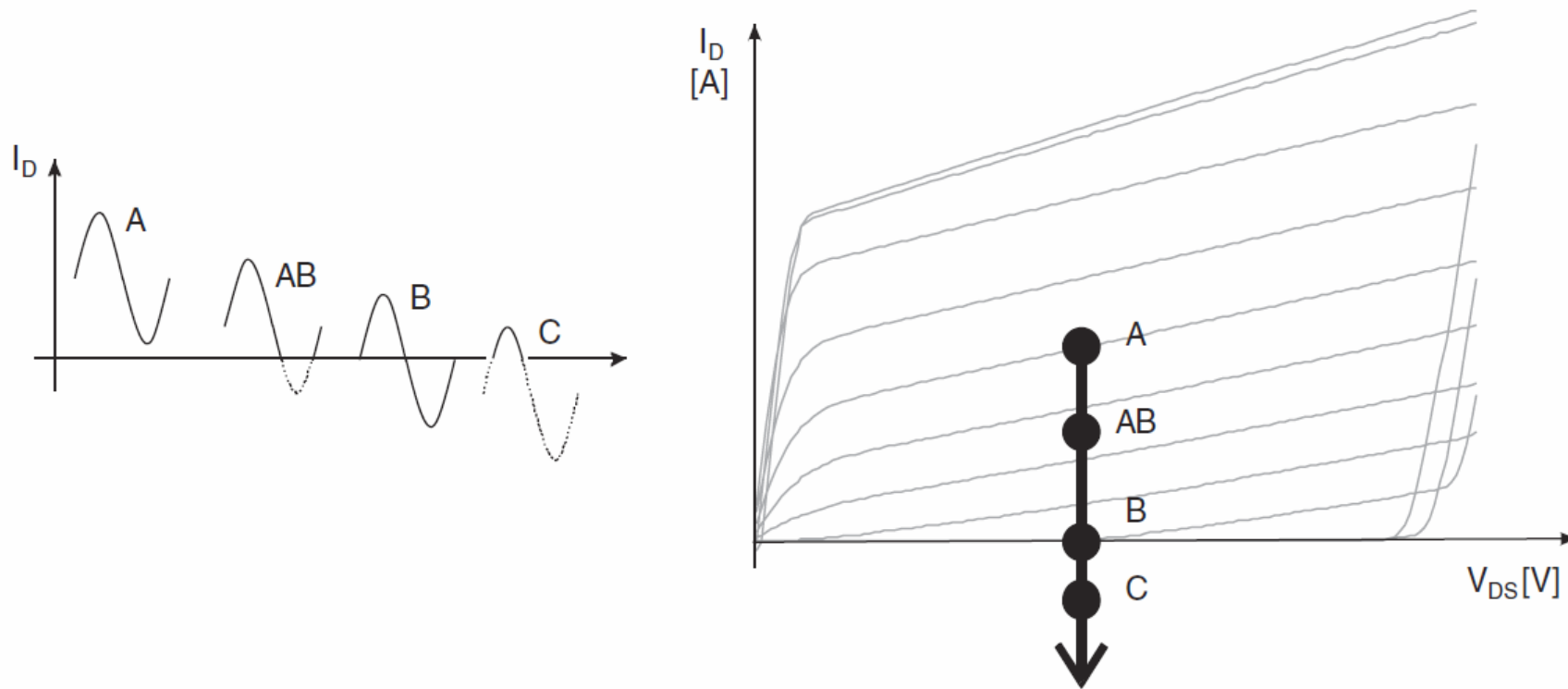


Biasing: 'Classic' Amplifier Classes

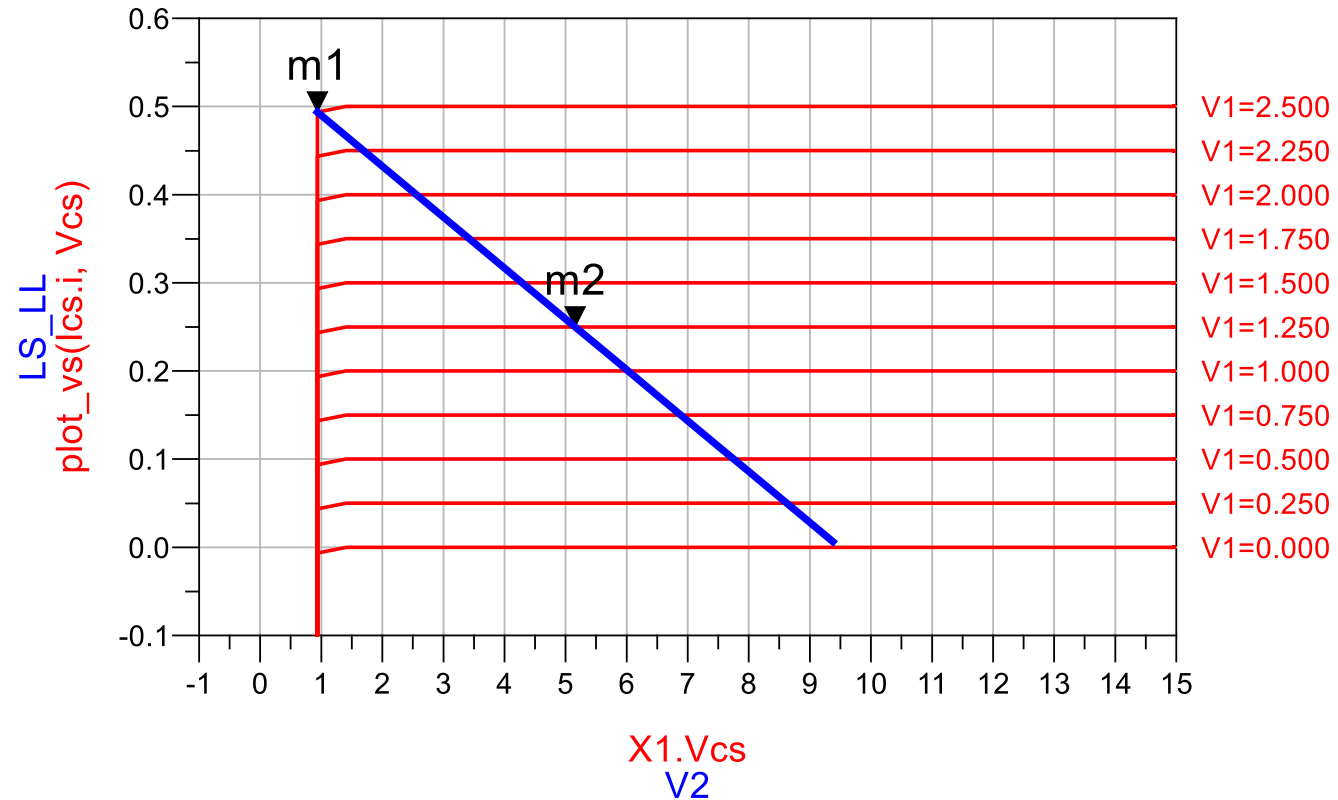

Biasing: 'Classic' Amplifier Classes

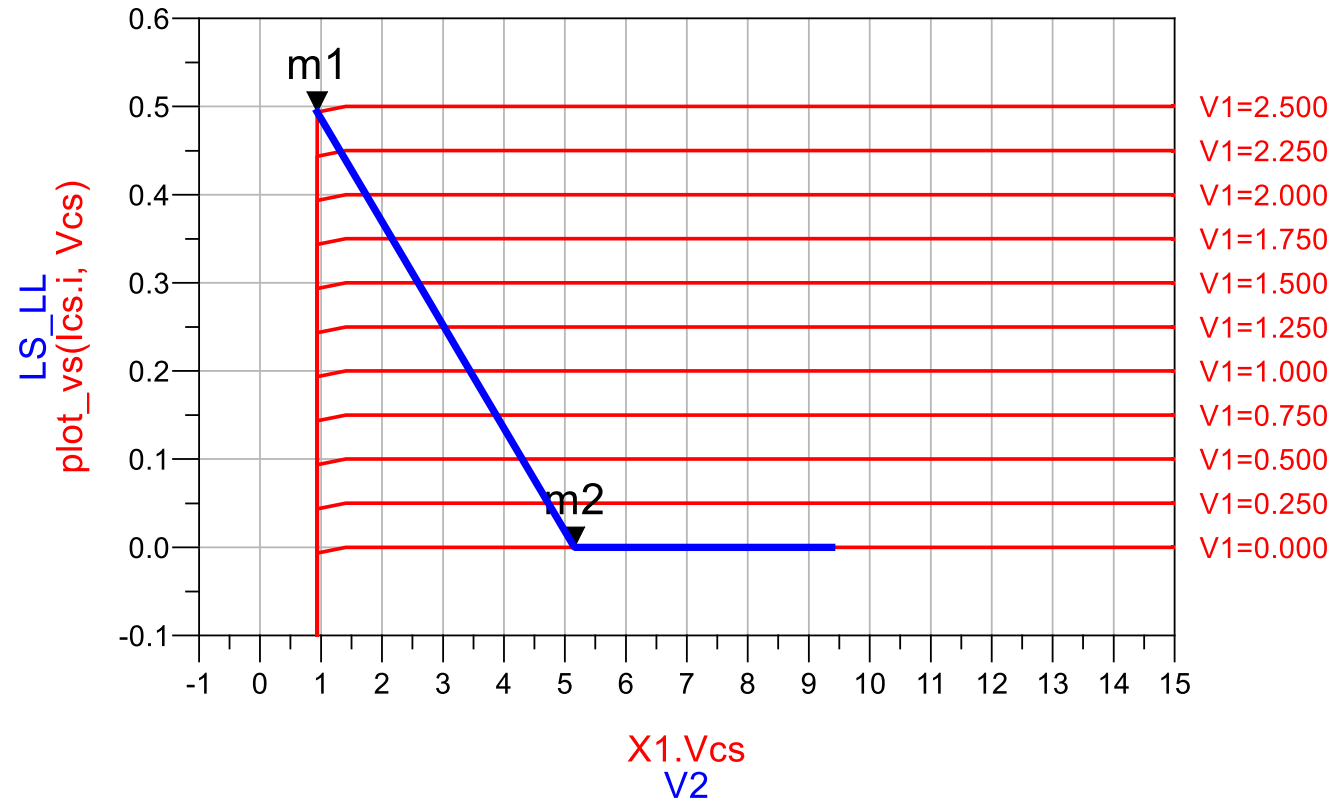

Generalised PA Architecture – Class AB

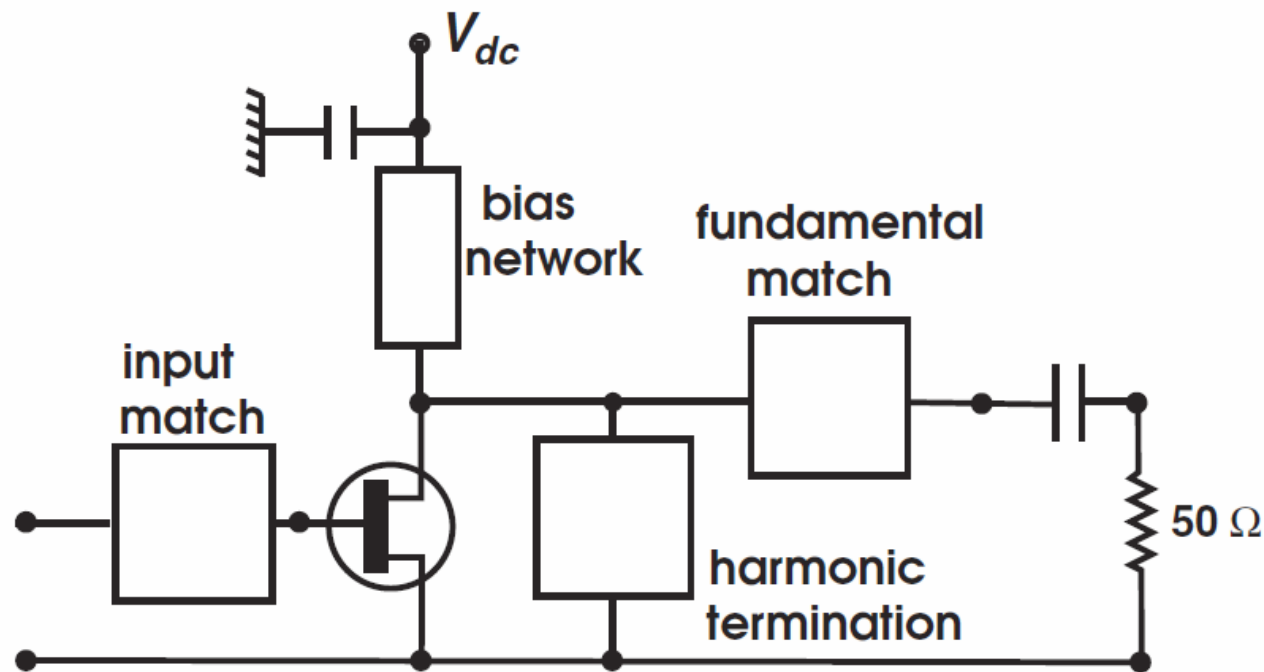


Cripps, S., 2012. Amplifier Classes, A to S. In: Walker, J. ed, 2012. *Handbook of RF and Microwave Power Amplifiers*. 1st ed. Cambridge: Cambridge University Press, Ch. 4, Fig. 4.9.

Simulation Controllers



- The type of simulation controllers is important – They dictate what circuit analysis you can do
- For QucsStudio:
 - DC – Fundamental
 - AC – Linear (small-signal)
 - Transient – Solves a set of differential equations that express time dependence of I's and V's of circuit
 - **S-Parameter**
 - **Harmonic Balance**
 - Parameter Sweeps (used with other controllers)
 - *Missing Envelope Simulation - Fast and complete analysis of complex signals such as digitally modulated RF signals, has advantages for some applications*
- QucsStudio can only run one controller at a time

S-Parameters

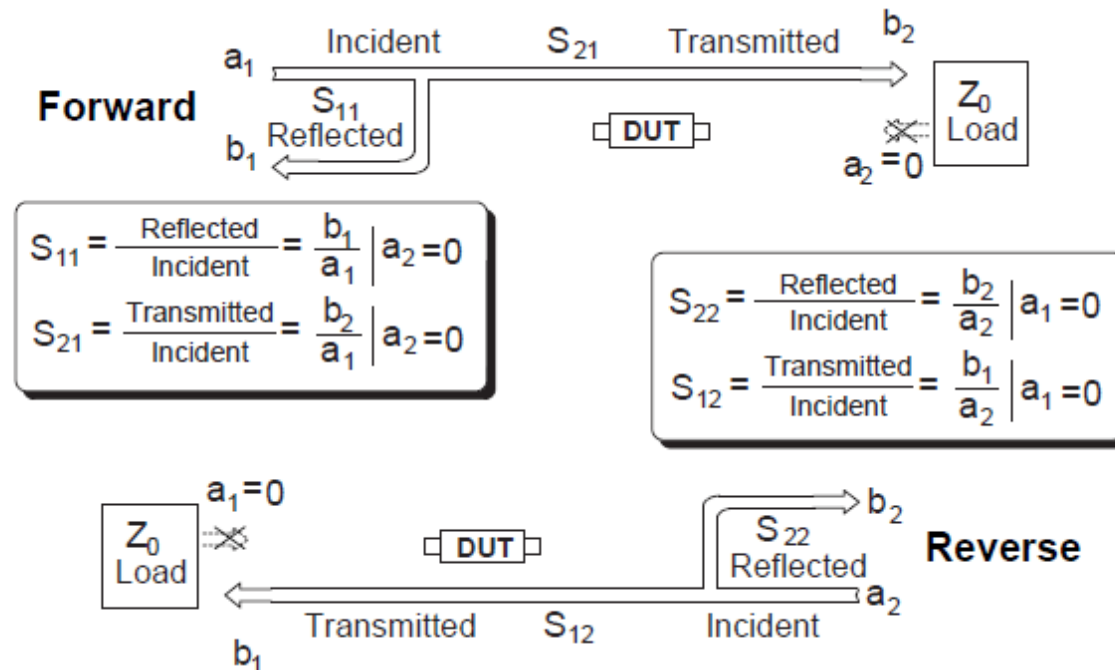- Widely used by industry and amateurs alike
- Ratio measurements, not absolute measurements
- LINEAR



S-Parameters

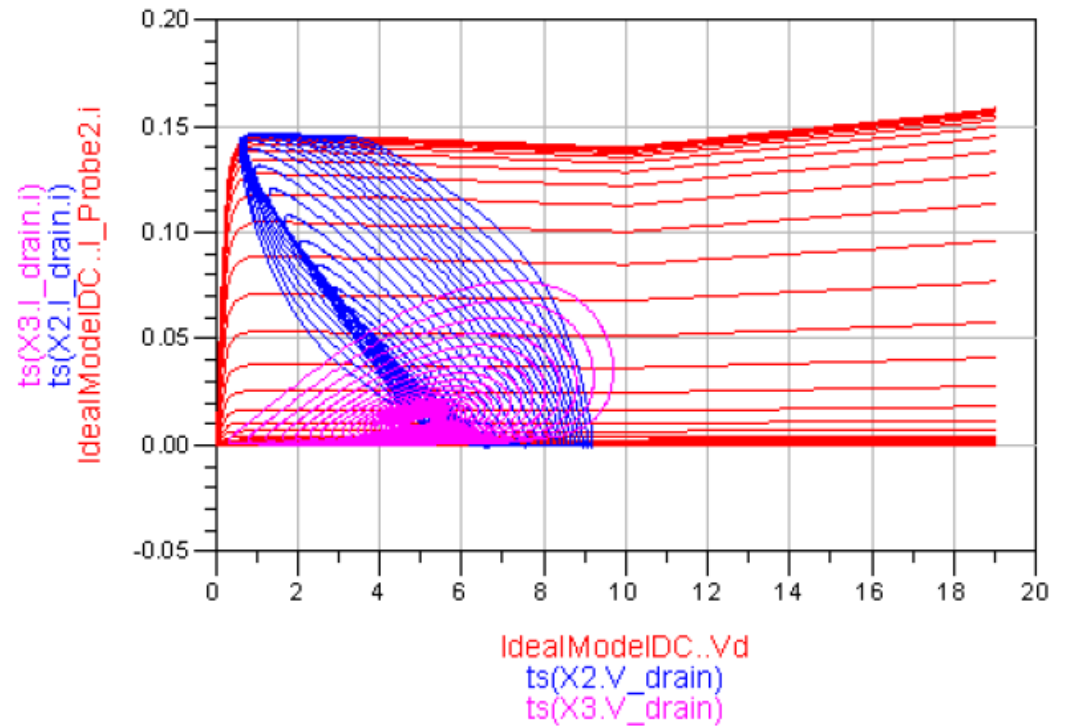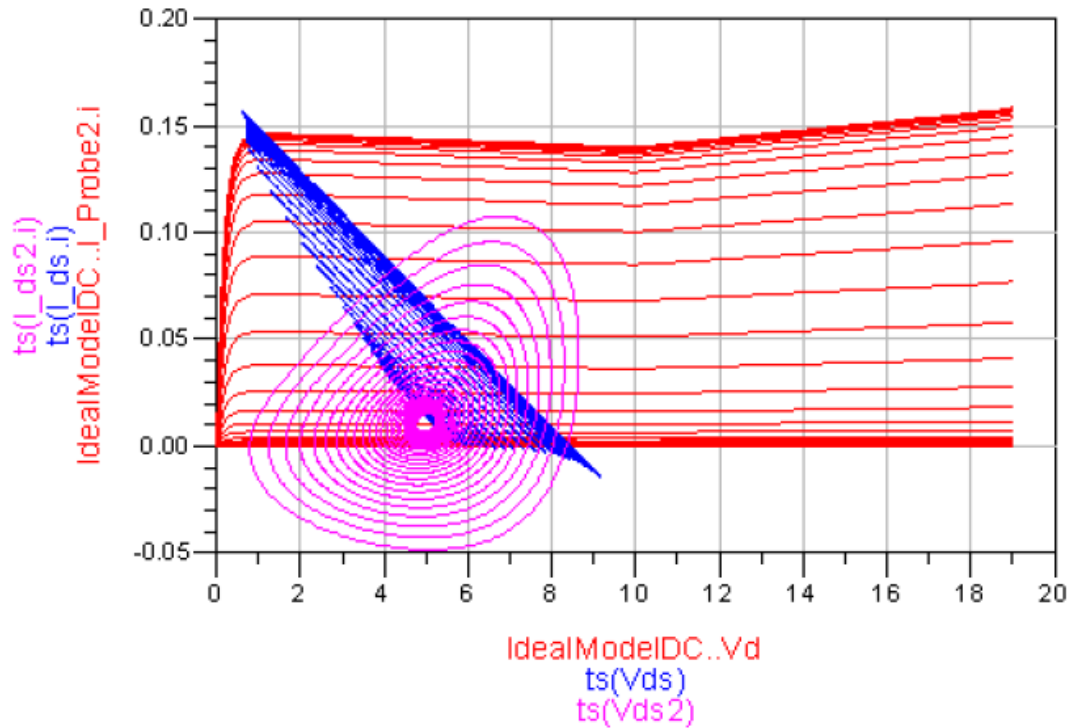

- (Pink) Reverse measurement, (Blue) Forward measurement
- (Left) Extrinsic, (Right) Intrinsic

Smith Chart Tool

- Automated Smith chart tool greatly reduces speed of designing matching networks
- SimSmith is a free tool for this purpose
- Available at: <http://www.w0qe.com/SimSmith.html>

TLine Calculator Comparison

- Compared QucsStudios Transmission Line Calculator to ADS LineCalc
- Used a Rogers RT/Duroid 5880 to calculate a microstrip line:
 - 2GHz
 - $\epsilon_r = 2.20$
 - $\tan\delta = 0.0009$
 - Substrate Thickness = 0.508mm
 - Conductor Thickness = 35um

LineCalc Tool


The image displays the LineCalc Tool interface, which is part of QucsStudio. The tool is used for calculating the properties of a microstrip line. The interface is divided into several sections:

- Physical Parameters:** W = 1.519590 mm, L = 27.422900 mm.
- Calculated Results:** $K_{\text{Eff}} = 1.867$, $A_{\text{DB}} = 0.025$, SkinDepth = 0.001.
- Substrate Parameters:** Er = 2.200, Mur = 1.000, H = 0.508 mm, Hu = 3.9e+34 mil, T = 35.000 μm , Cond = 4.1e7, TanD = 9.000e-4, Rough = 0.000 mil, DielectricLossModel = 1.000, FreqForEpsrTanD = 10.0e9, LowFreqForTanD = 1.0e3, HighFreqForTanD = 1.0e12.
- Component Parameters:** Freq = 2.000 GHz, Wall1, Wall2.
- RF Properties:** Z0 = 50 ohms, Angle = 90 degree.
- Results:** Skin Depth: 1.75756 μm , $\epsilon_{r,\text{eff}}$: 1.86605, Conductor Losses: 0.0302481 dB, Dielectric Losses: 0.00521485 dB, Radiation Losses: 0.0049413 dB, Single-Mode Range: 0 Hz ... 58.6 GHz.

The 3D diagram shows a microstrip line on a substrate with width W, length L, thickness T, and height H.


QucsStudio – Ideal Transistor

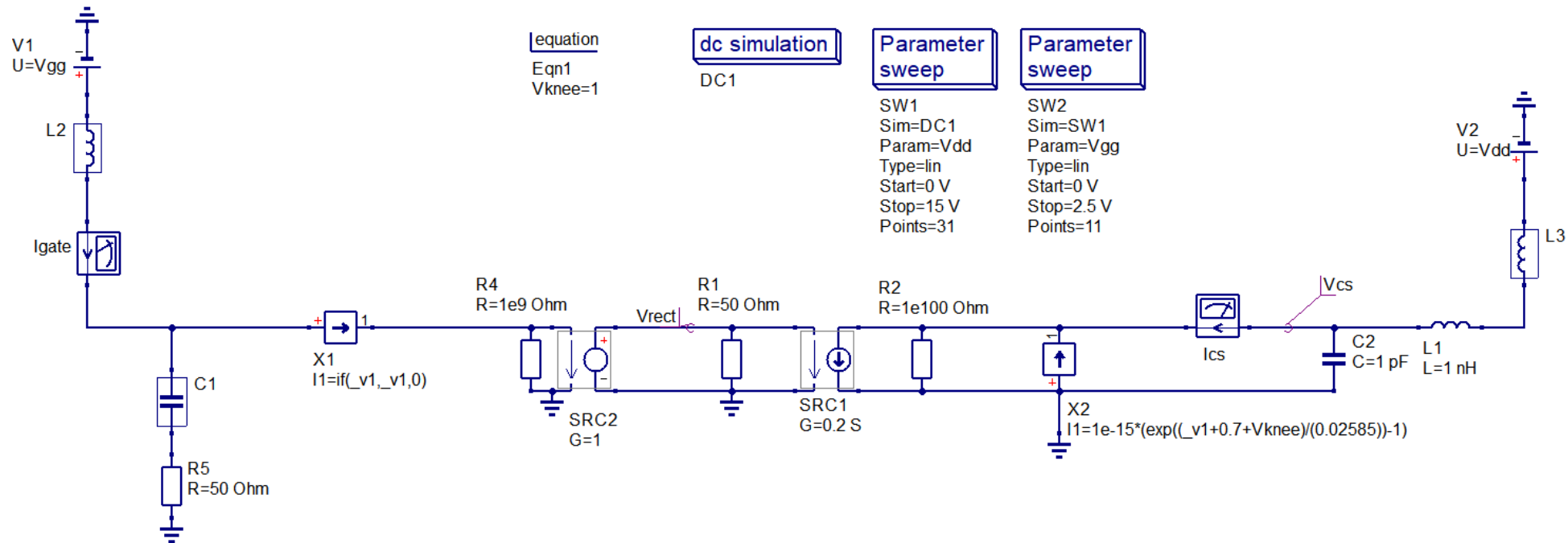- DC-IV simulation of ideal transistor (can specify V_{knee} and gain)




QucsStudio – DC-IV Plot

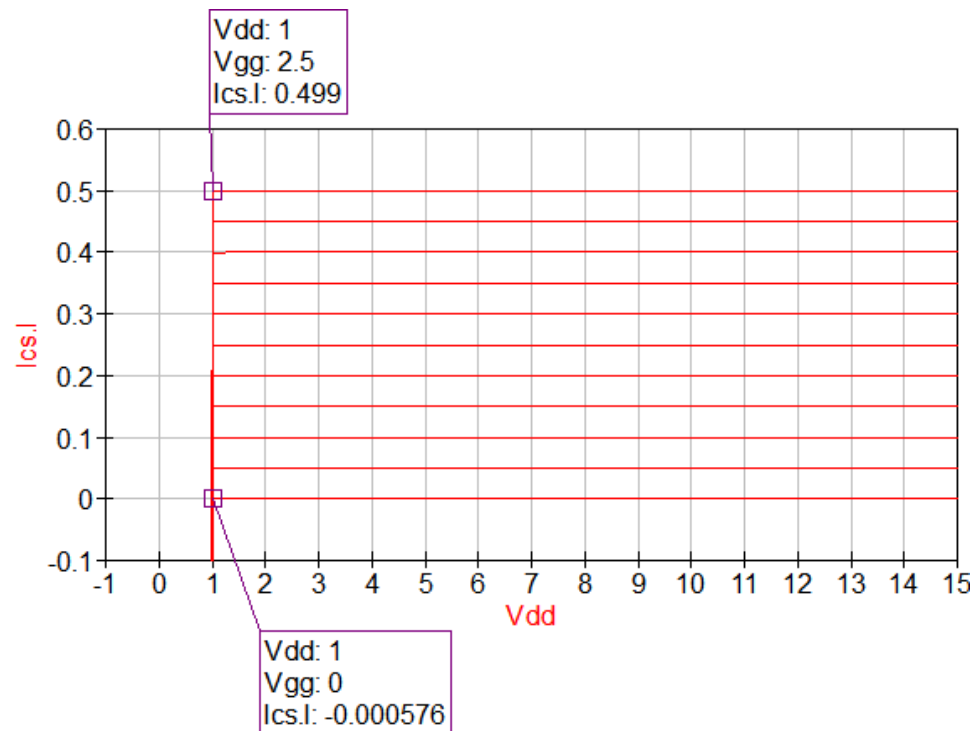- $V_{knee} = 1V$ and $I_{max} = 0.5A$
- Plotted using QucsStudio's inbuilt data display tool



QucsStudio – Class B Amplifier

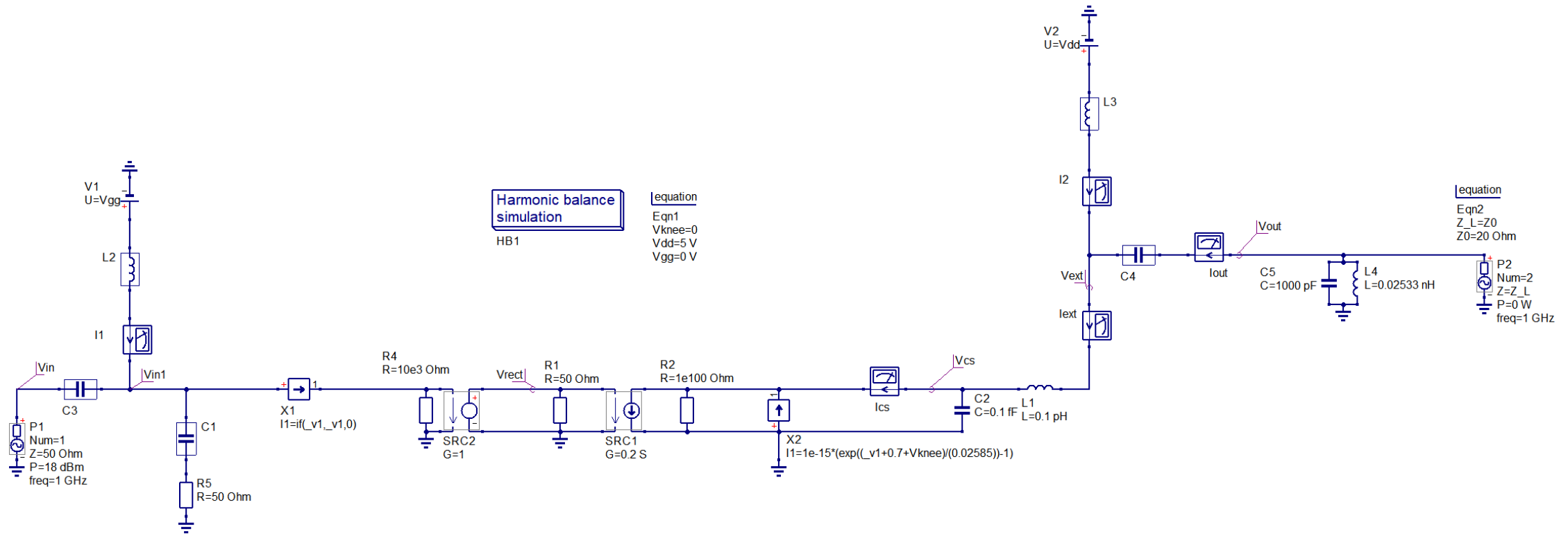- Ideal 'Class B' waveforms produced by biasing the transistor appropriately (specify V_{gg} as shown)



QucsStudio – Octave Script



- Harmonic Balance simulation performed for ideal Class B amplifier shown in previous slide
- Problem: Frequency-domain data produced, want to plot the ideal waveforms (convert results to time-domain)
- One solution: Octave scripts can be integrated into QucsStudio (and other Qucs branches)! Write script to perform Inverse-Fast Fourier Transforms (IFFTs) on I and V data and plot it
- **Octave integration gives complete control over data manipulation and display**

QucsStudio – Octave Script

- Write script in Octave then set data display in QucsStudio to use the resulting .m file

```
CUARS_Talk_3.m x
1 # Post-processing script for circuit simulation file "CUARS_Talk_3.sch"
2 # Plots the current and voltage waveforms at the current generator plane
3
4 freq = loadQucsVariable("CUARS_talk_3.dat", "hbfrequency");
5 Ics = loadQucsVariable("CUARS_talk_3.dat", "Ics.Ib");
6 Vcs = loadQucsVariable("CUARS_talk_3.dat", "Vcs.Vb");
7
8 padding_size = 2^10;
9
10 time = 1/freq(2);
11 time = time * (1e9); # Convert to ns
12
13 # ---- Calculate and plot Ics waveform ----
14 # FFT coefficients w/o zero padding, with negative freq values
15 wave_Ics_fl = [Ics(1) rot90(Ics((2:end))/2) rot90(conj(Ics((end:-1:2))/2))];
16 wave_Ics_fl = [Ics(1) rot90(Ics((2:end))/2) zeros(1, (padding_size - length(wave_Ics_fl))) rot90(conj(Ics((end:-1:2))/2))];
17
18 # FFT coefficients, w/ zero-centered zero padding, with negative freq values
19 # # of zeros is calculated to produce a power-of-two # of total values
20 # by subtracting the original length of testwave_v2_fl
21 wave_Ics_t1 = ifft(wave_Ics_fl);
22 # Calculate and apply scaling to zero-padded iffts w/ respect to original ifft
23 wave_Ics_t1 = padding_size * wave_Ics_t1;
24 # Double waveform (for clarity when plotting), comment out and change t to be linspace between 0 and 1 to have just one cycle
25 wave_Ics_t1 = [wave_Ics_t1 wave_Ics_t1];
26
27 # Plot waveform
28 t = linspace(0,2*time,length(wave_Ics_t1));
29 figure(1);
30 plot(t, wave_Ics_t1, 'b');
31 xlabel('Time (ns)');
32 ylabel('Current (A)');
33
34 # ---- Calculate and plot Vcs waveform ----
35 # FFT coefficients w/o zero padding, with negative freq values
36 wave_Vcs_fl = [Vcs(1) rot90(Vcs((2:end))/2) rot90(conj(Vcs((end:-1:2))/2))];
37 wave_Vcs_fl = [Vcs(1) rot90(Vcs((2:end))/2) zeros(1, (padding_size - length(wave_Vcs_fl))) rot90(conj(Vcs((end:-1:2))/2))];
38
39 # FFT coefficients, w/ zero-centered zero padding, with negative freq values
40 # # of zeros is calculated to produce a power-of-two # of total values
41 # by subtracting the original length of testwave_v2_fl
42 wave_Vcs_t1 = ifft(wave_Vcs_fl);
43 # Calculate and apply scaling to zero-padded iffts w/ respect to original ifft
44 wave_Vcs_t1 = padding_size * wave_Vcs_t1;
45 # Double waveform (for clarity when plotting), comment out and change t to be linspace between 0 and 1 to have just one cycle
46 wave_Vcs_t1 = [wave_Vcs_t1 wave_Vcs_t1];
```

QucsStudio – Octave Script

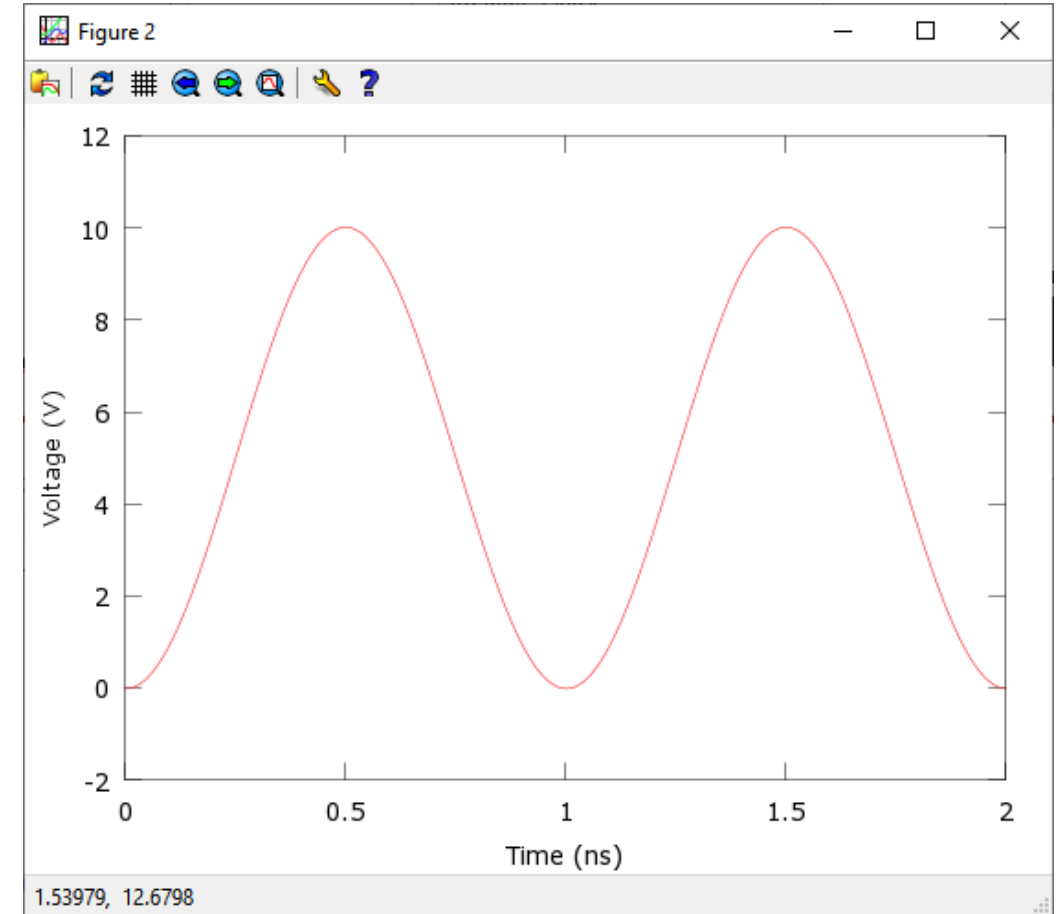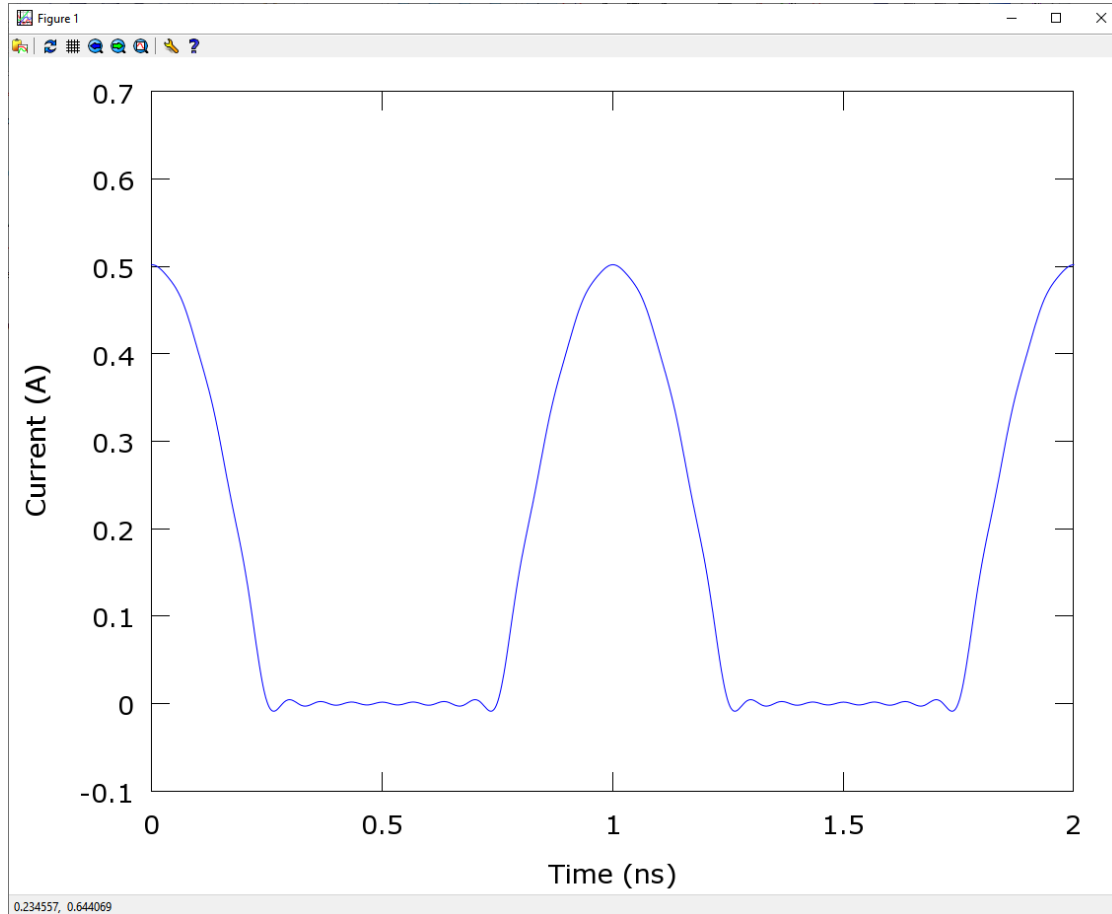

QucsStudio – Octave Script

- These QucsStudio examples are definitely work-in-progress, they simply prove that there is a lot of untapped potential
- Should be possible to extend the Octave script to include a GUI (sliders ect) and plot the load-line, giving data display capabilities approaching commercial software equivalents
- ‘Under-the-hood’ there is more capability available in QucsStudio ect. than shown right now but it is not particularly easy to use (especially for beginners)
- **A reminder: The files will be available on our website (<https://www.cardiffars.org.uk/>) – Please contribute to improving this!**

Conclusions

- Free tools are available and can be useful
- Steeper learning curve, particularly if you have no prior experience
- Steadily being improved
- You can help right now through creating example workspaces for learning: **Share your knowledge!**

Conclusions

Questions?