
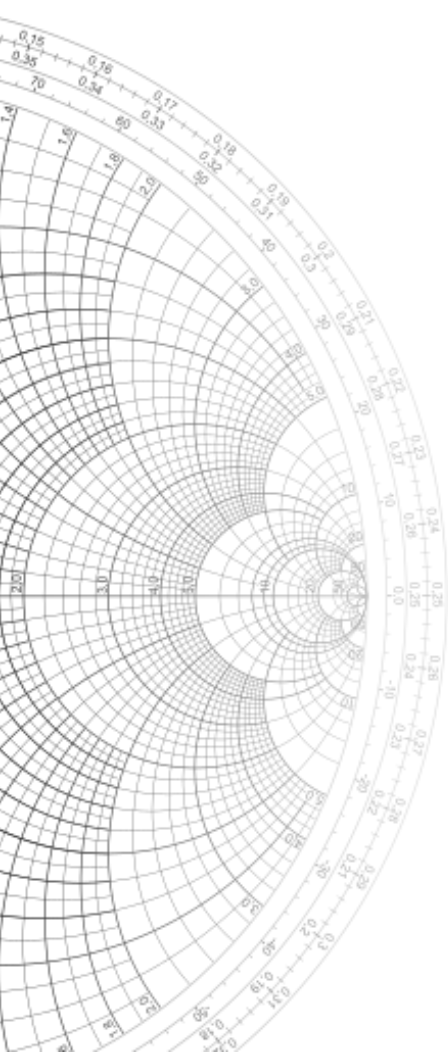
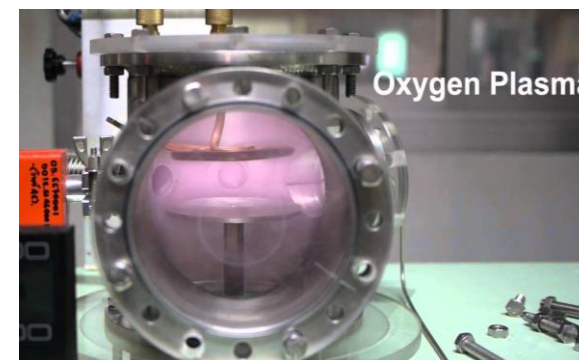
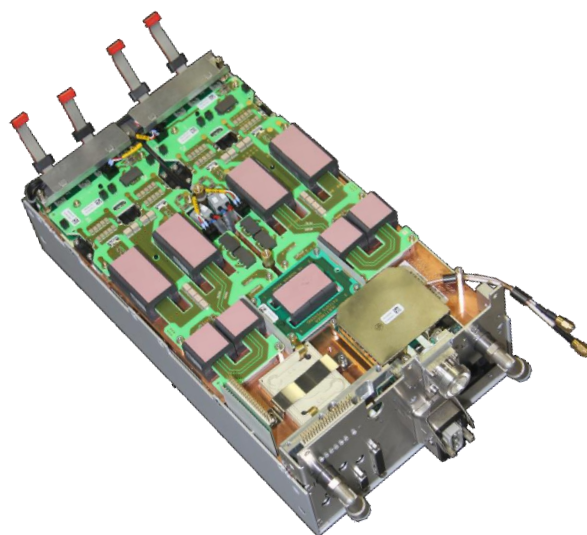
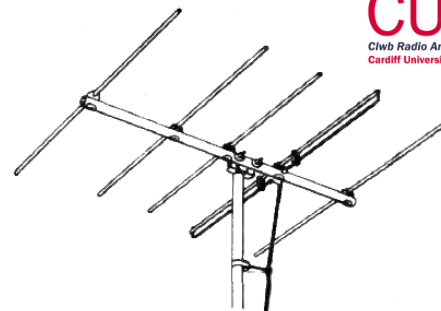
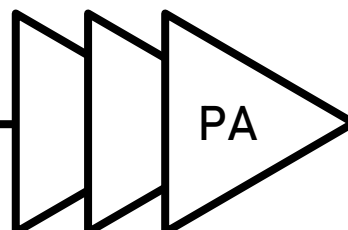
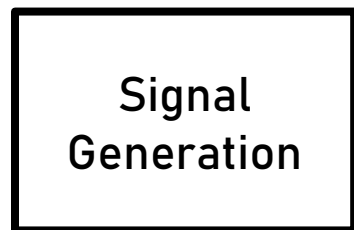


Transistor Load Lines


Contents

- 
- What are load lines
 - Why are they useful
 - How to measure them
 - PA classes
 - Using in PA design
 - Advanced
 - Class F
 - Load modulation/supply modulation
 - Rectifiers


Motivation

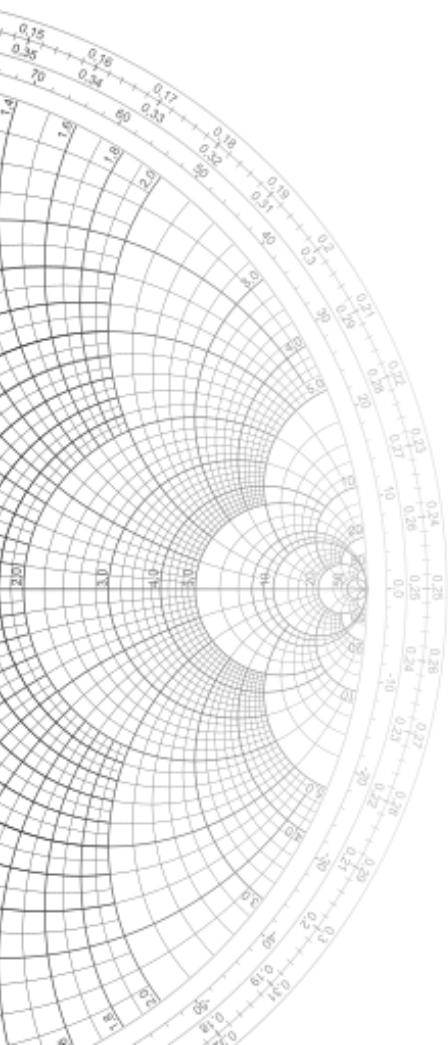

PAs

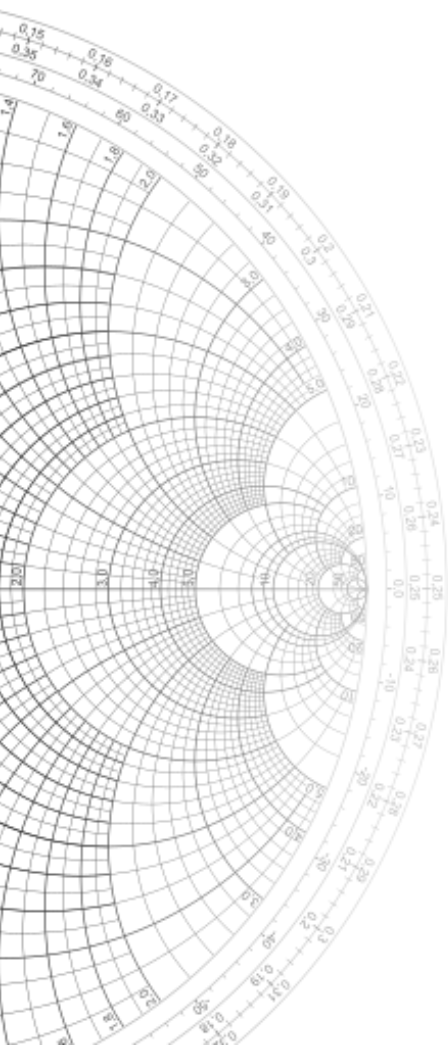


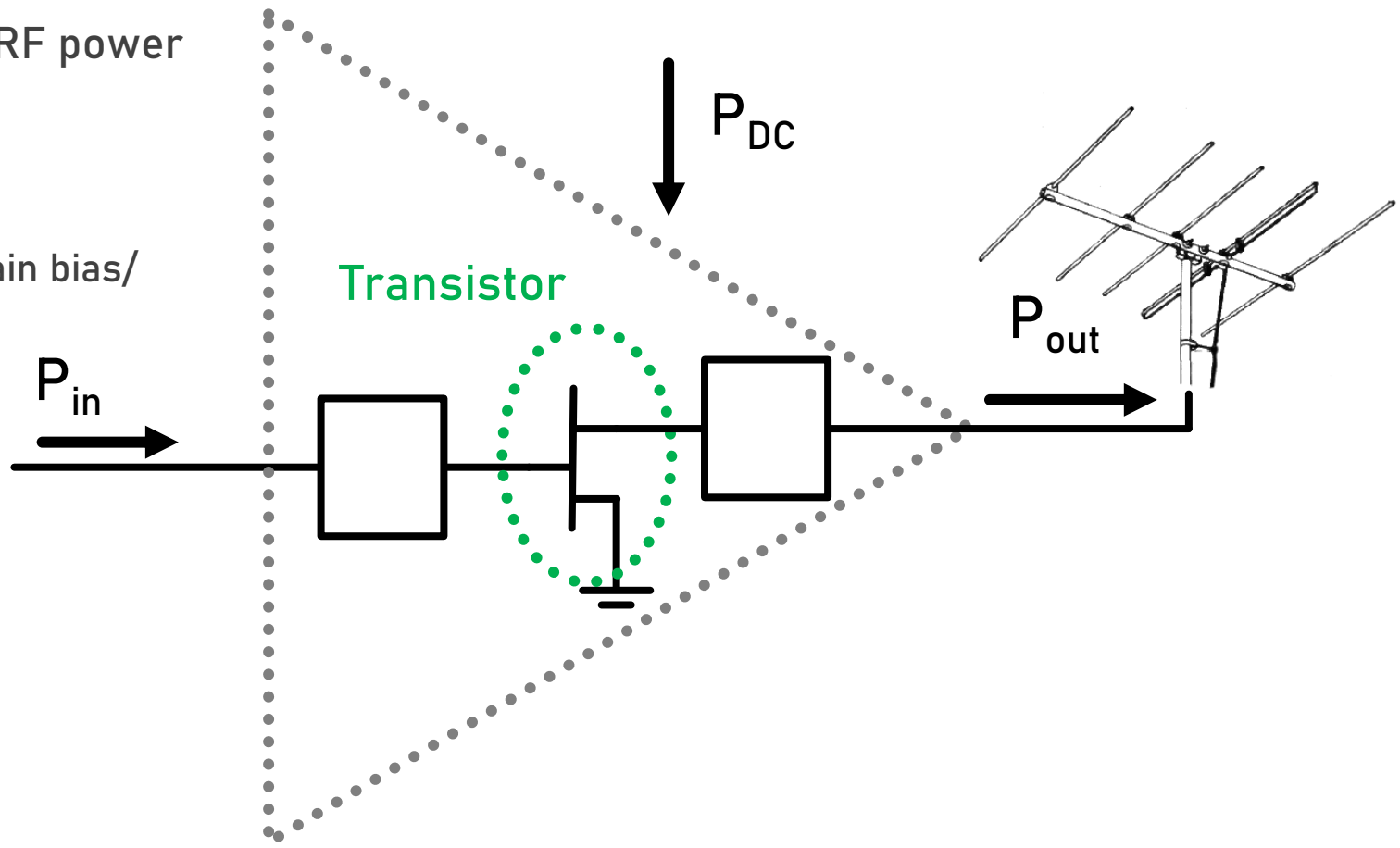- Amplify RF signal
- Convert DC power to RF power
- Inputs:
 - RF input power
 - DC input power/ Drain bias/ Supply voltage
 - Gate bias
- Outputs:
 - RF output power
 - Heat!





PAs

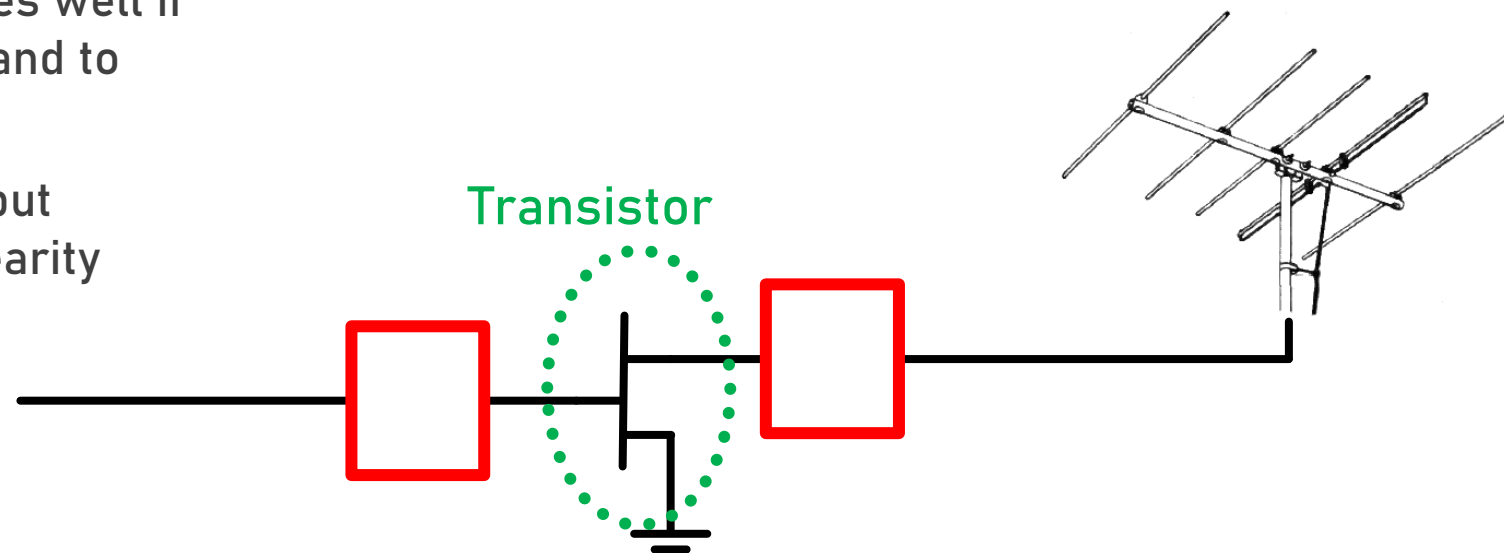- Important part: Matching Networks
- Make sure PA operates well if connected to source and to load
- Determines gain, output power, efficiency, linearity




Matching networks

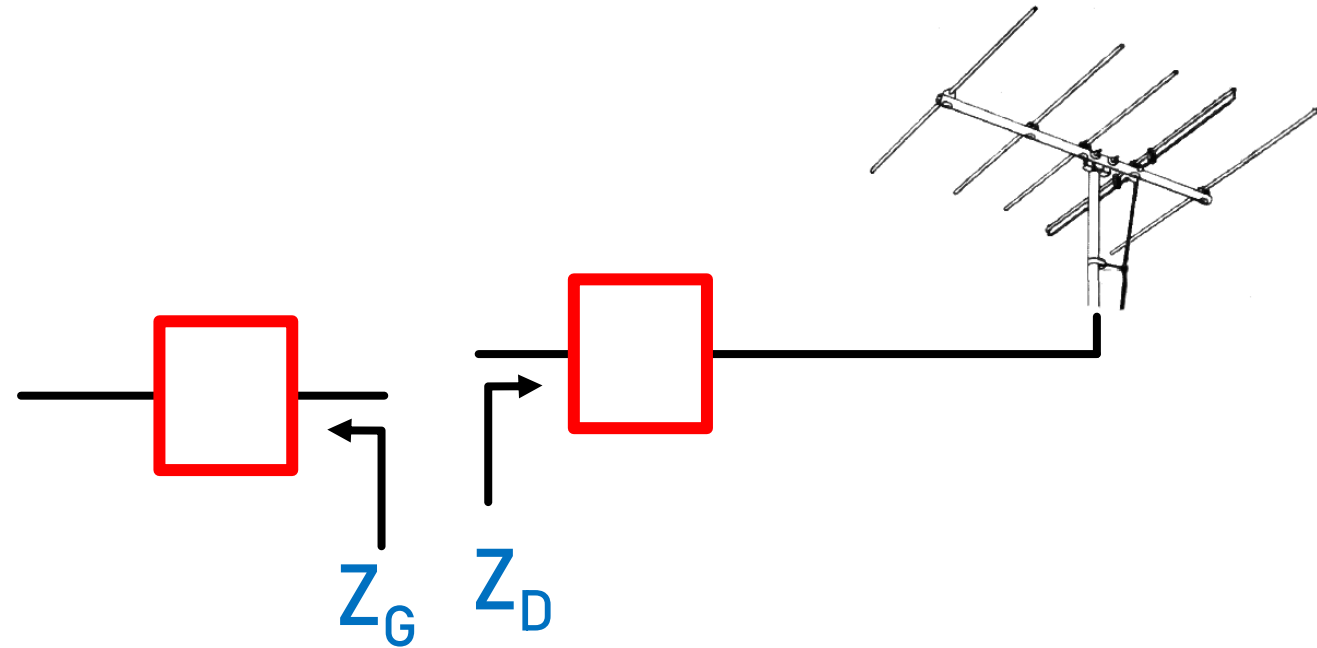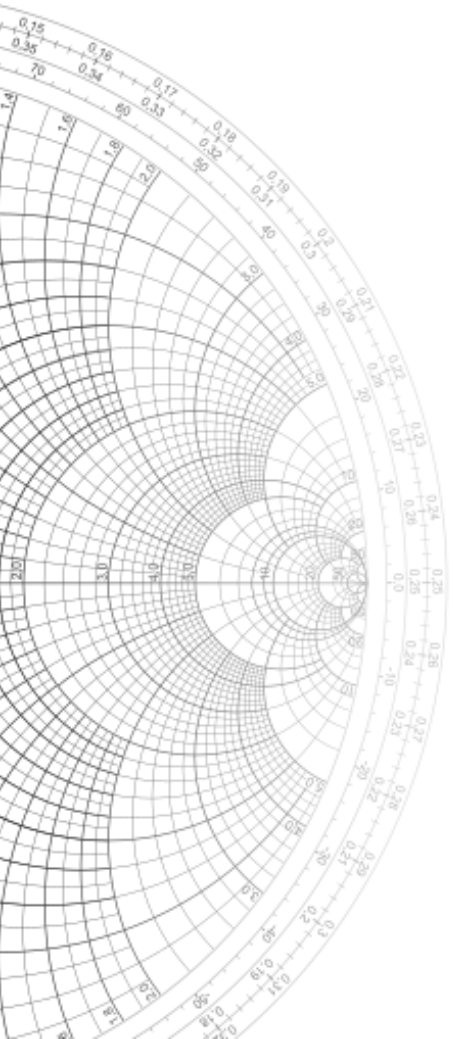- Need to know impedances
- Might be in data sheet
- Eval board might be available
- If model available and usable, can do load-pull simulation (or ask someone else to do it)
- If no good model, can do load-pull measurement (or ask someone)



Transistor

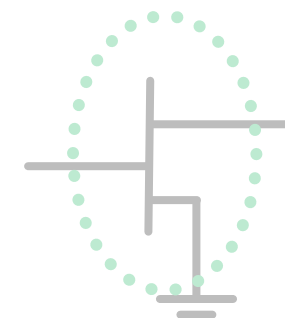


7


IV Curves

- Take step back and look at transistor
- IV show how current behaves for combinations of gate and drain voltage
- 3 regions

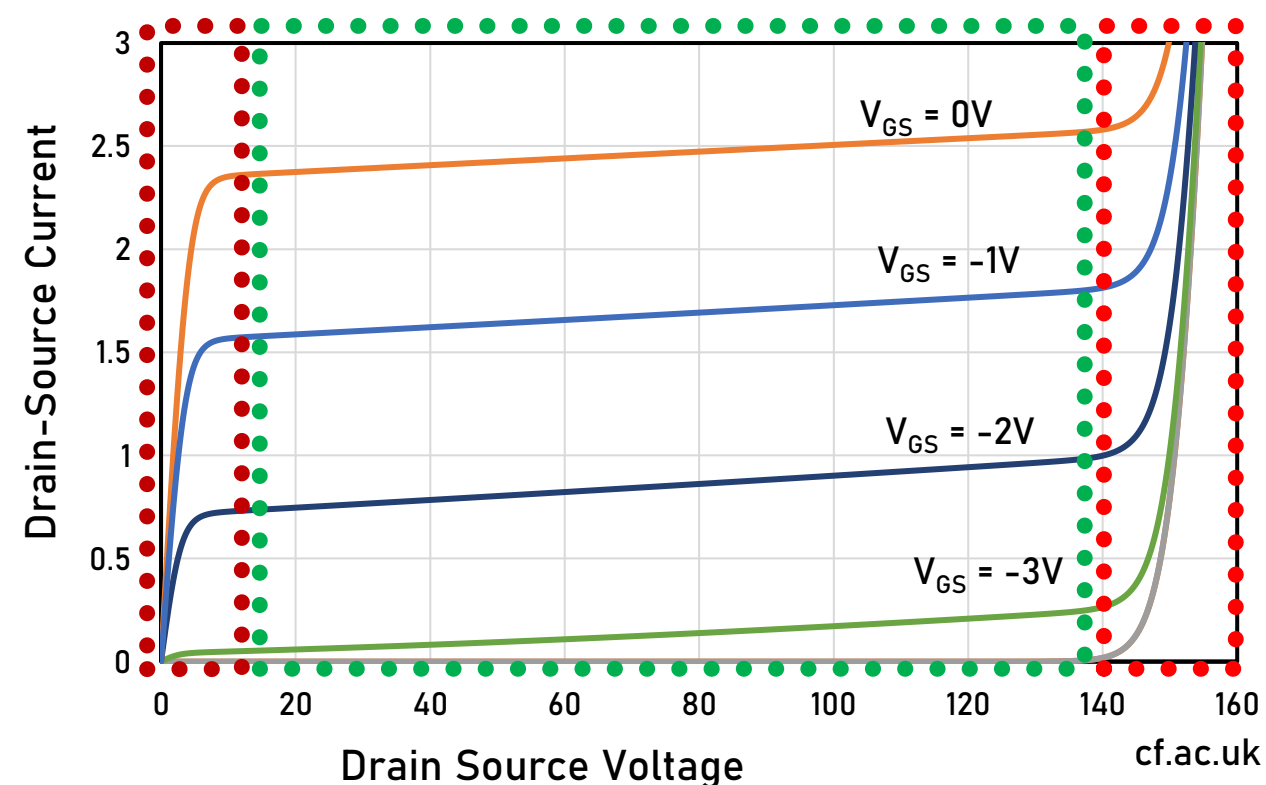- Linear region**, transistor behaves like resistor, funnily enough the transistor isn't very linear here
- Saturation region**, current depends mostly on gate voltage
- Breakdown region**
Don't be here






Transistor

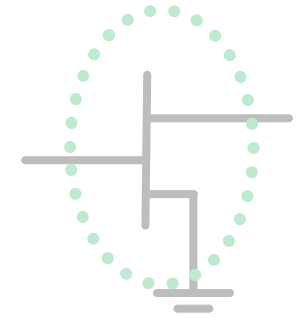



Enter Load-Lines

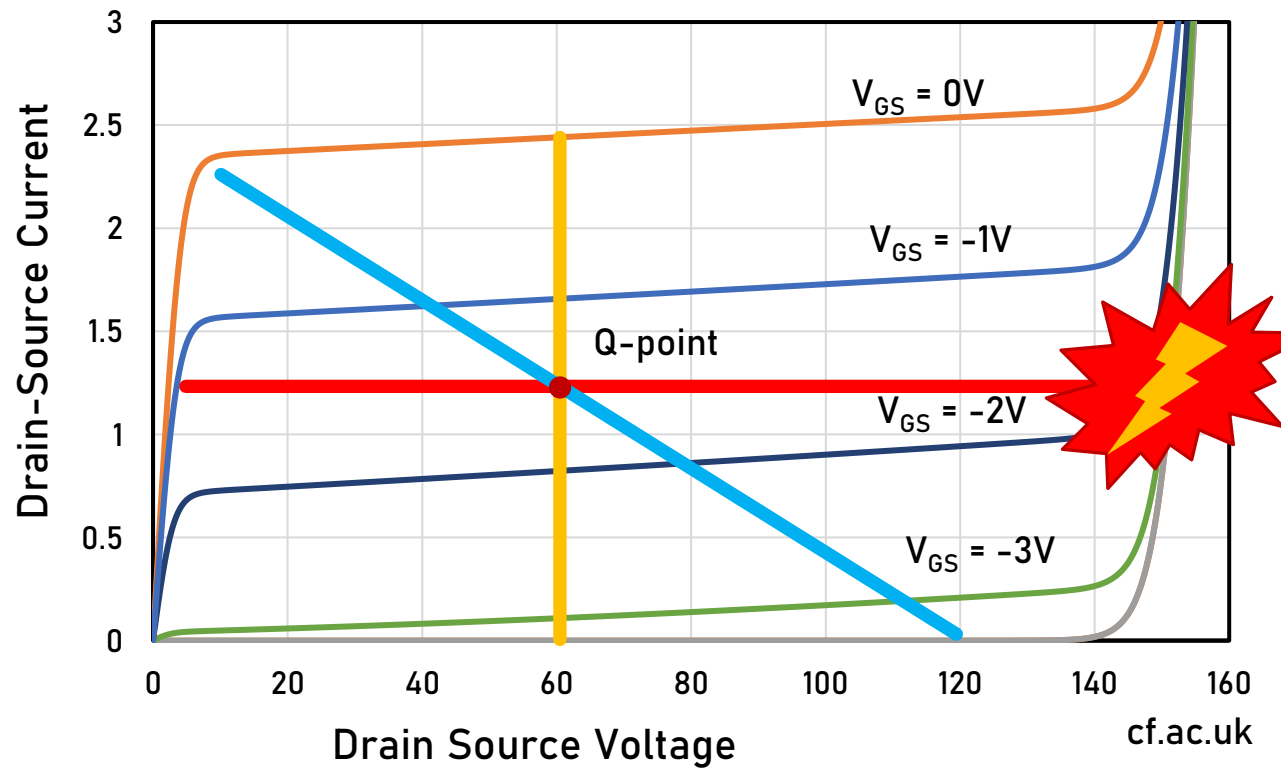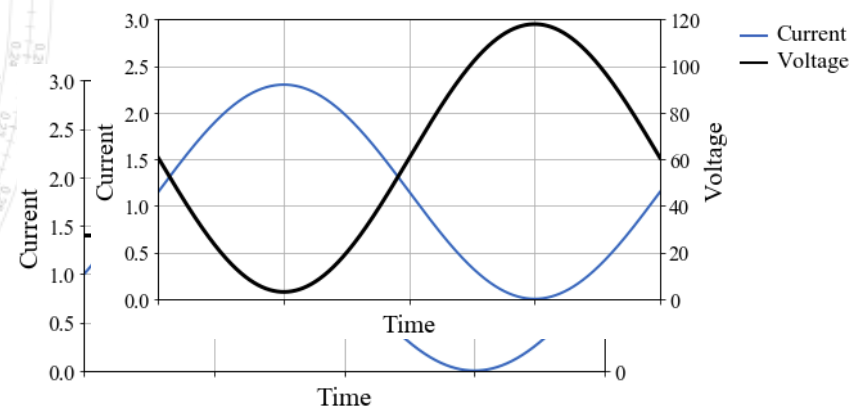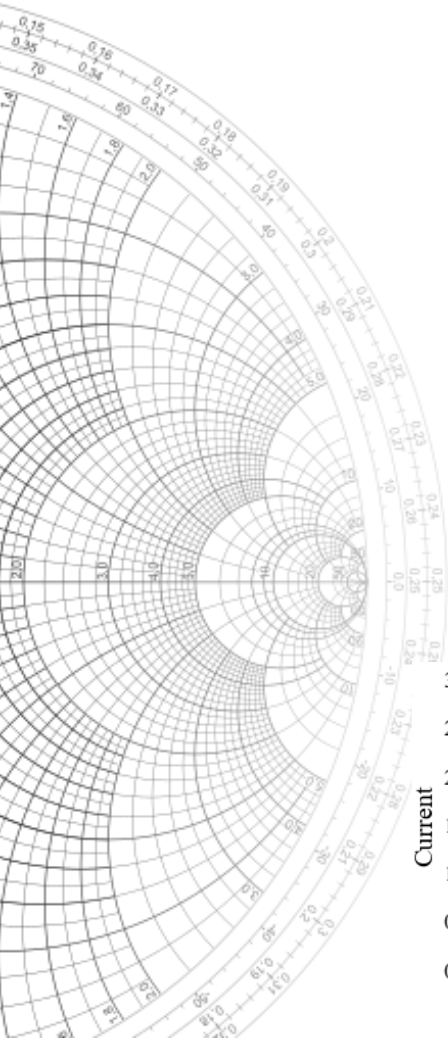- By changing the gate voltage, the drain current changes -> Controlled current source (surprisingly good model!)
- Voltage developed as a result depends on load impedance
- Load line plots voltage vs current, both in one trace
- Quiescent current determines the point around which the load lines form





PA classes - Class A

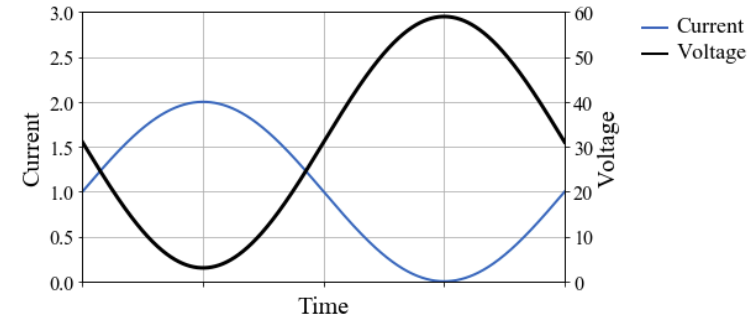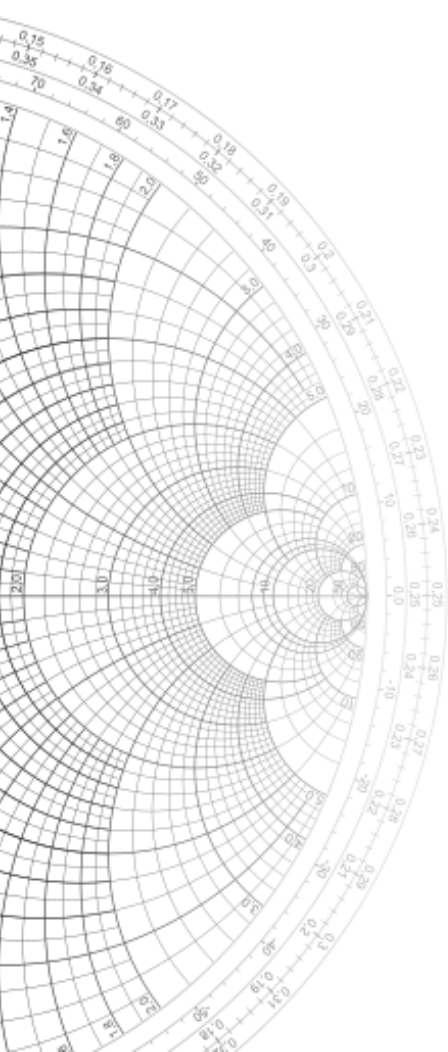- Remember
 - $P = V * I$
 - Transistor dissipates power at all points in time!
- But!
- Super linear
- All of the gain
- Amazing if we
 - Can get the heat away
 - Don't have to foot the energy bill






Transistor

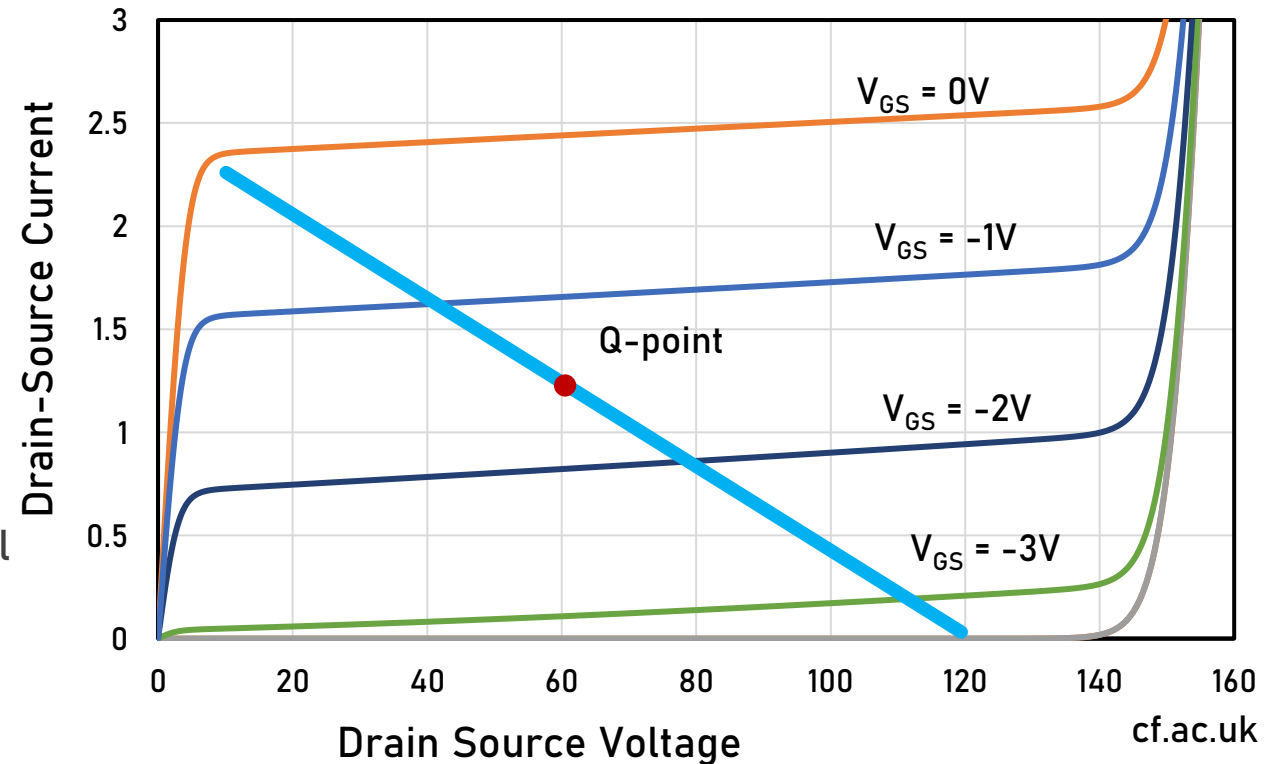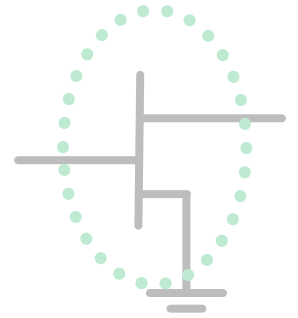

PA classes - Class B


- Same load impedance as class A but load line looks different!
- Assumes perfect short circuit of harmonics
- Transistor has no losses for half the time (ideally)
- Still fairly linear
- Starts at 0 current, needs twice the gate voltage swing -> 6dB less gain

Transistor

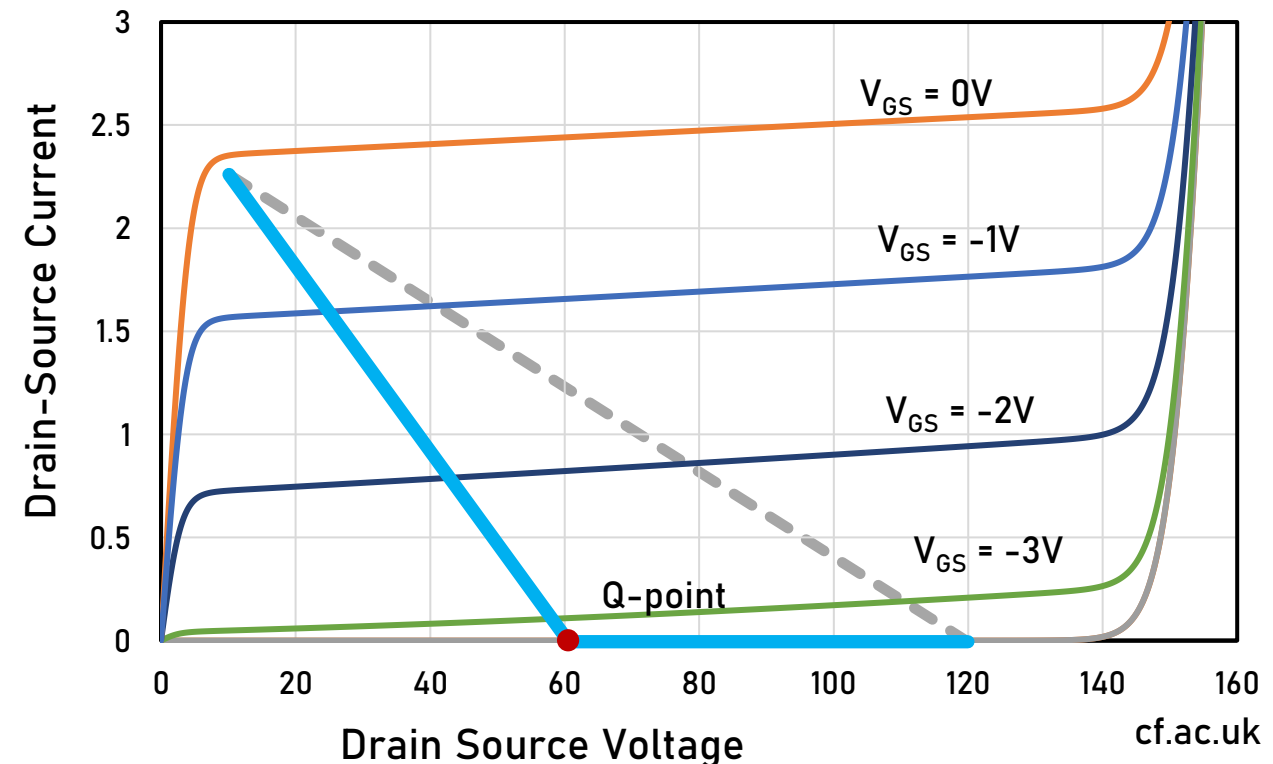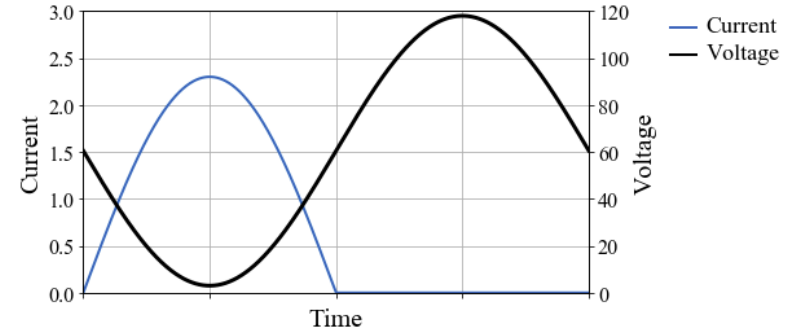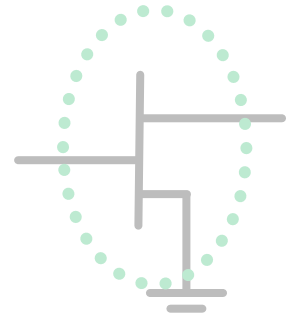


Measuring IV curves

- ▶ Very simple measurement:
 - ▶ Two adjustable voltage sources
 - ▶ One multi-meter to measure the current (plus a second one if you don't trust your voltage source)
- ▶ V_D and V_G are swept and I_D is measured
- ▶ Need to make sure to stay clear of maximum power (ideally by a lot)
- ▶ Also need to stay clear of breakdown voltage (datasheet value is good enough)
- ▶ But: Not a big issue, interesting bit is around small drain voltages anyway (max current)

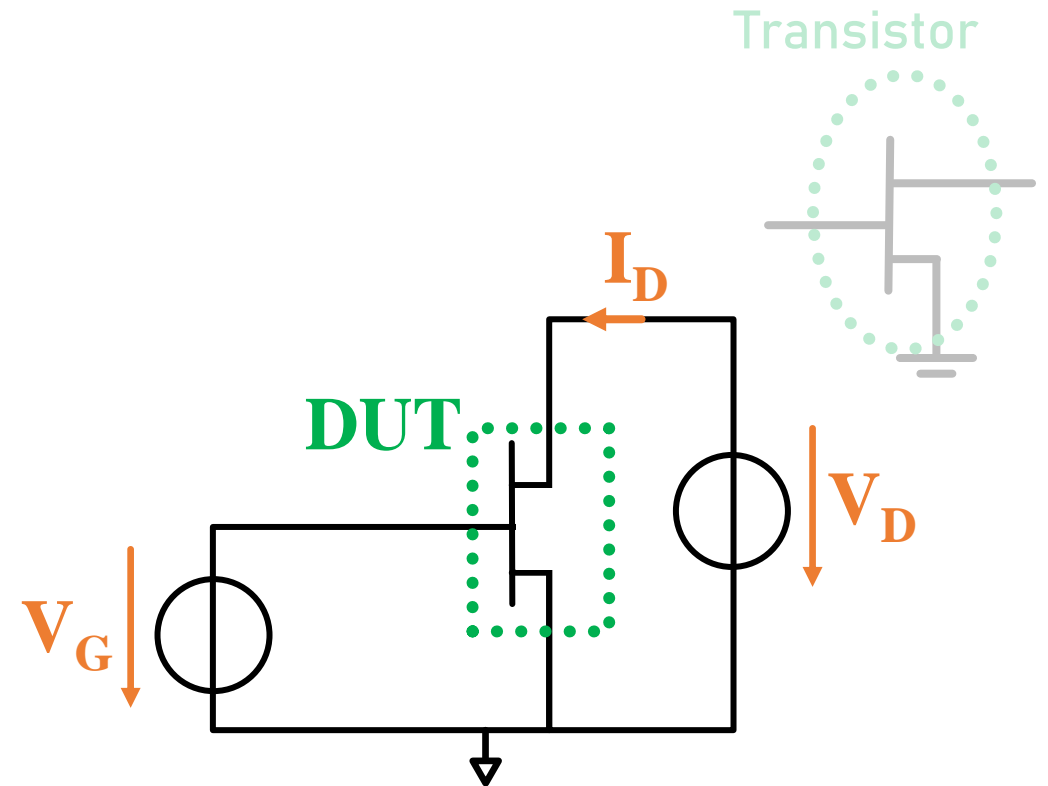


Measuring IV curves

Transistor

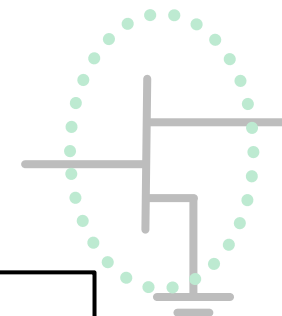


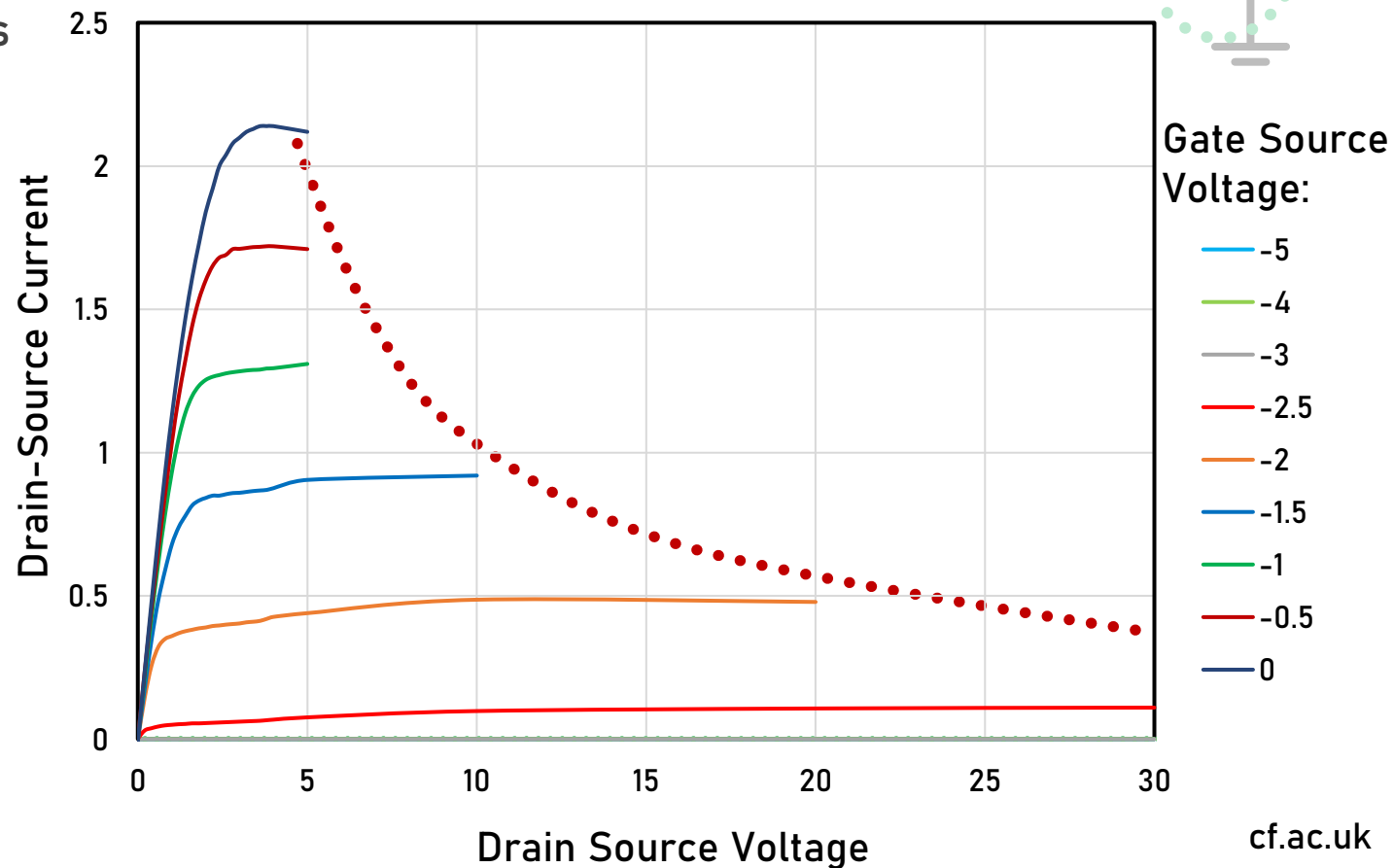
- Measurement result of Wolfspeed 10W GaN HEMT
- Maximum power depends on mounting
- Tried to stay below 10W



Measuring IV curves


- Measurement of a BF254C JFET
- Can directly design with the IV curves (depending on frequency)
- Can use them to fit a model (eg SPICE)

Transistor

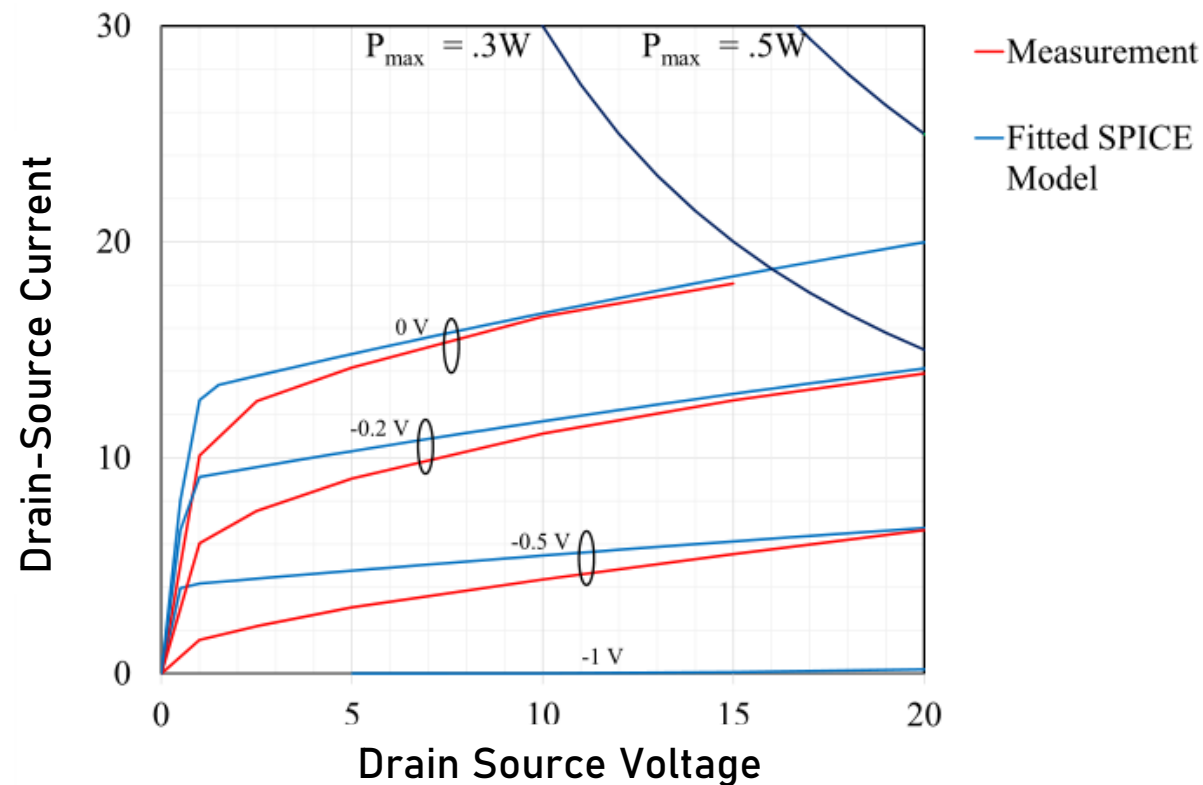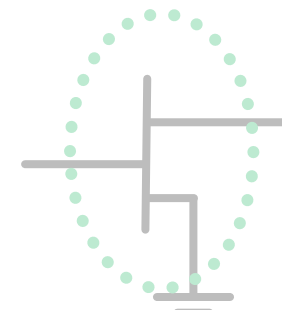


Matching networks

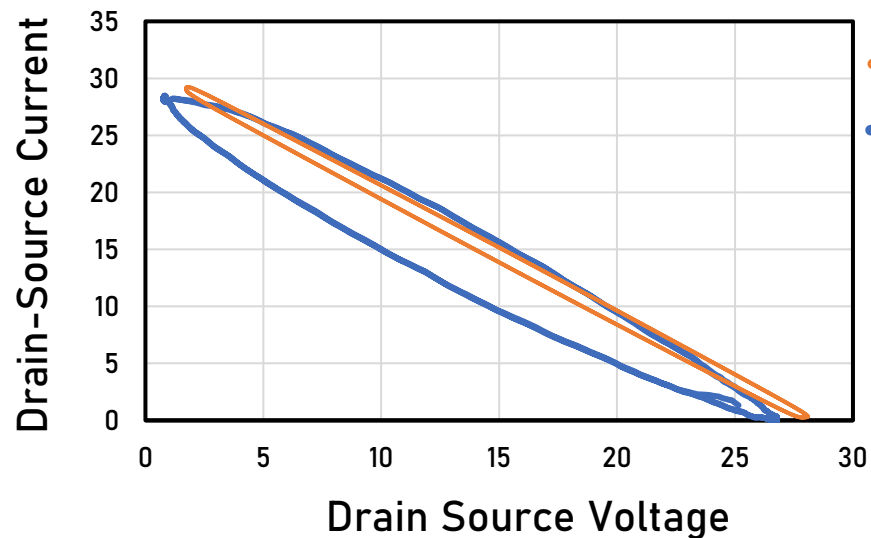- Using SPICE model or IV curves, matching circuit can be designed and simulated
- Simulation and measurement show good agreement
- The measured load line looks more like an oval...



— Simulation
— Measurement

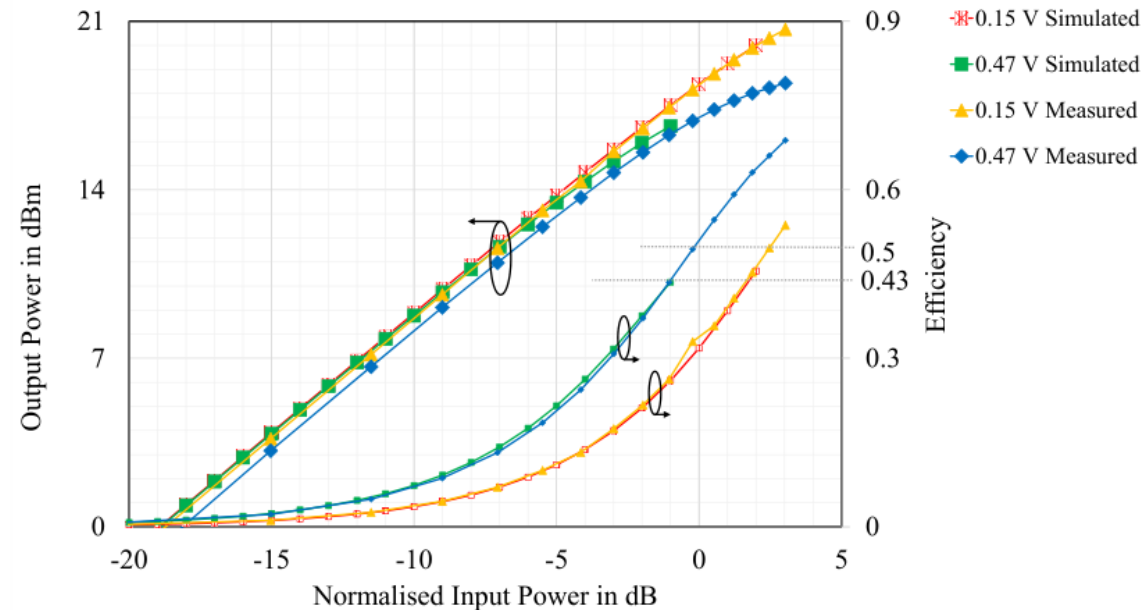

Not so fast!


- Sounds all nice and easy and:
- It can be (if we're lucky!)

But

- Physics getting in the way (as always)
- Transistors are more than just a current source
- Transistors are tiny
- GaN HEMTs start doing weird stuff


Not just a current source

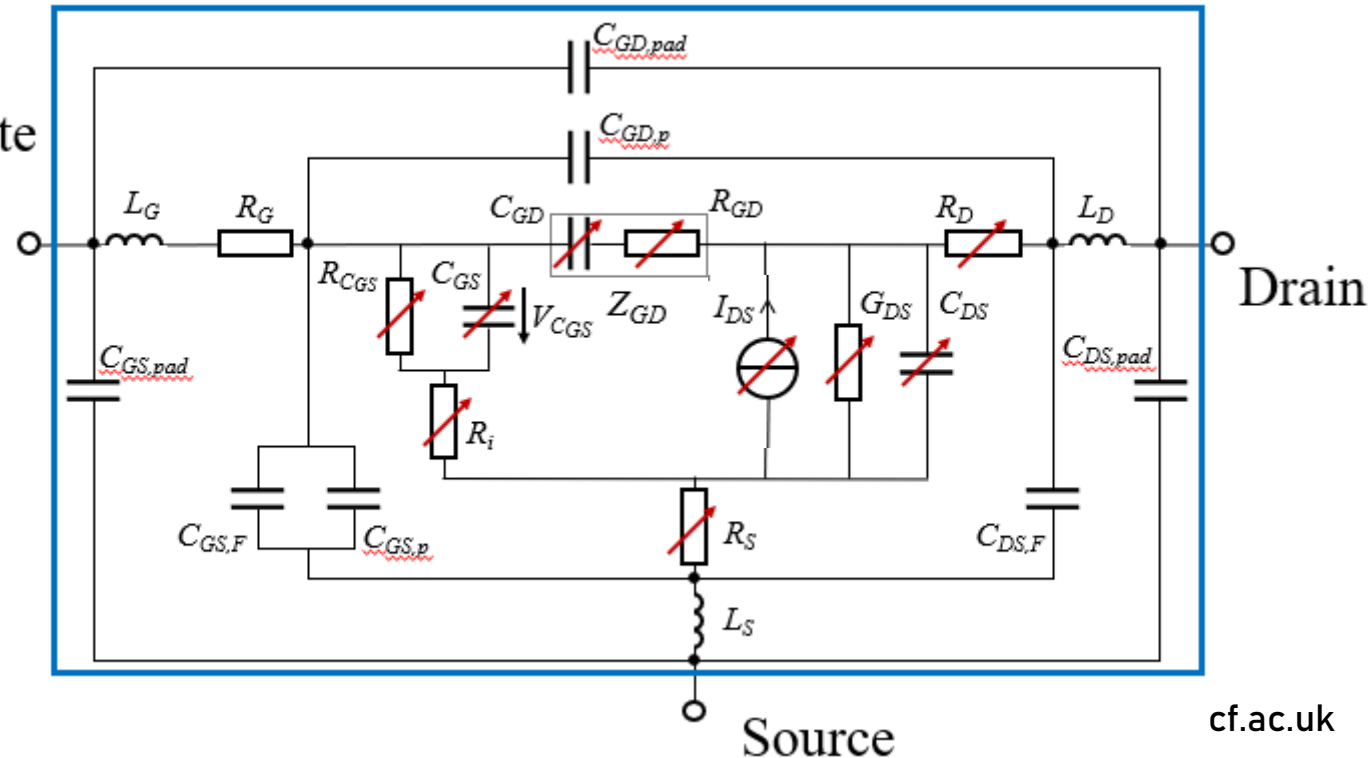- ▶ Transistors have lots of parasitic effects!
- ▶ Depending on frequency might not be that relevant
- ▶ Once it becomes relevant, need to deal with it
- ▶ If we're lucky someone else already did this and measured the parasitics
- ▶ If not we can make educated guesses or resort to load pull (or try manually optimising it)





Tiny transistors

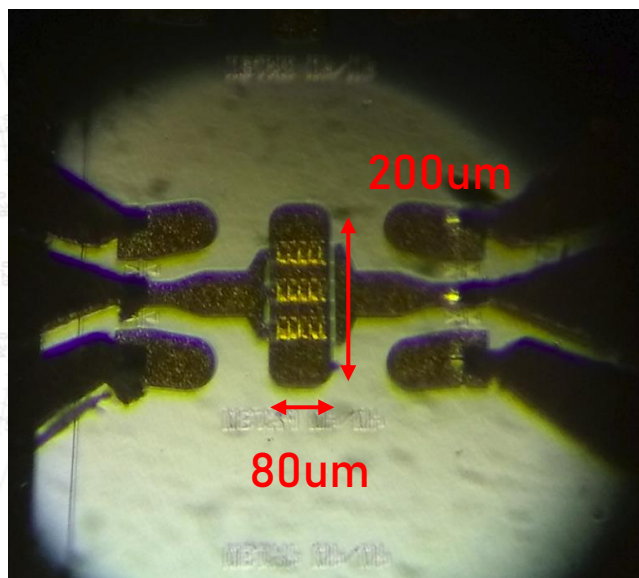
- Transistors are typically surprisingly small
- 2kW LDMOS is around 6mm x 25mm, 20W LDMOS .6mm x 2.5mm
- GaN HEMTs are even more compact
- Almost all transistors are packaged, adds more



3 W device

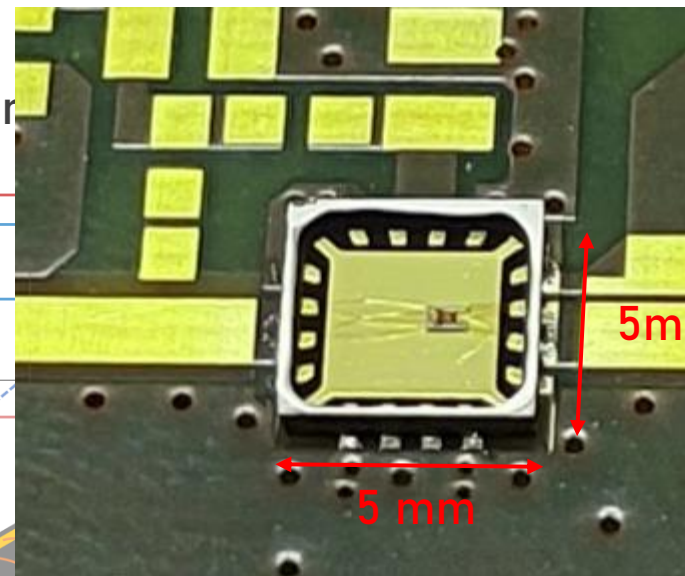
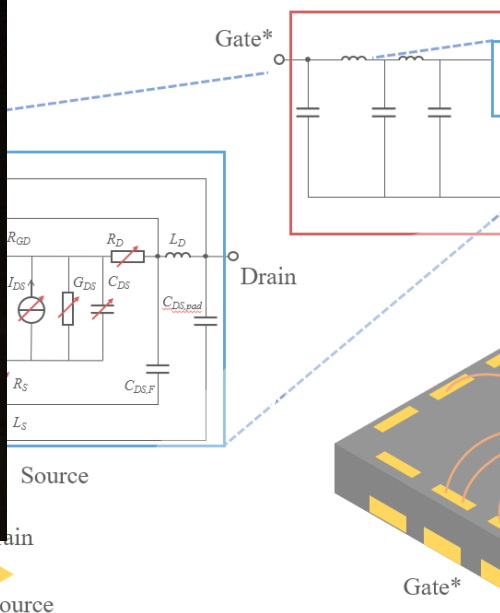


6 W device

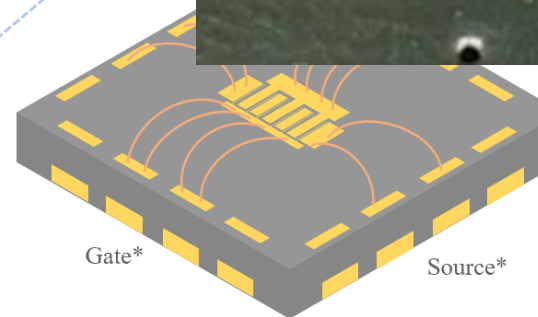

GaN transistors and the linear region


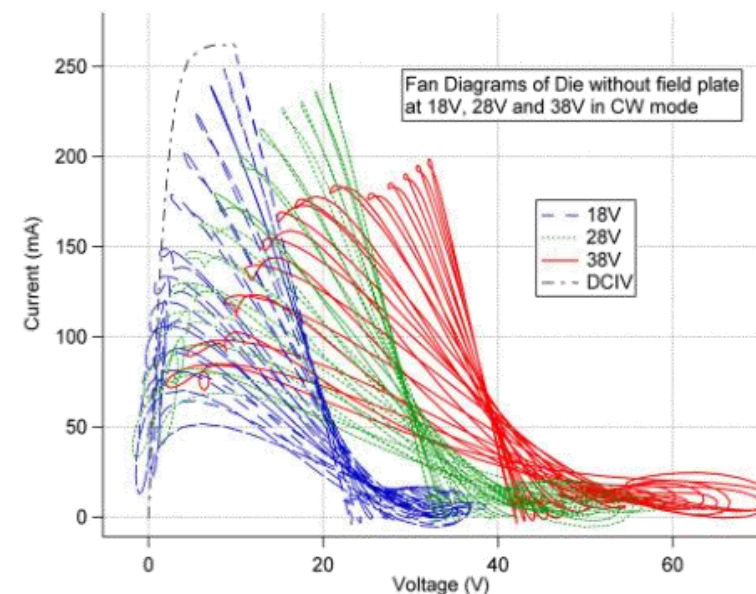
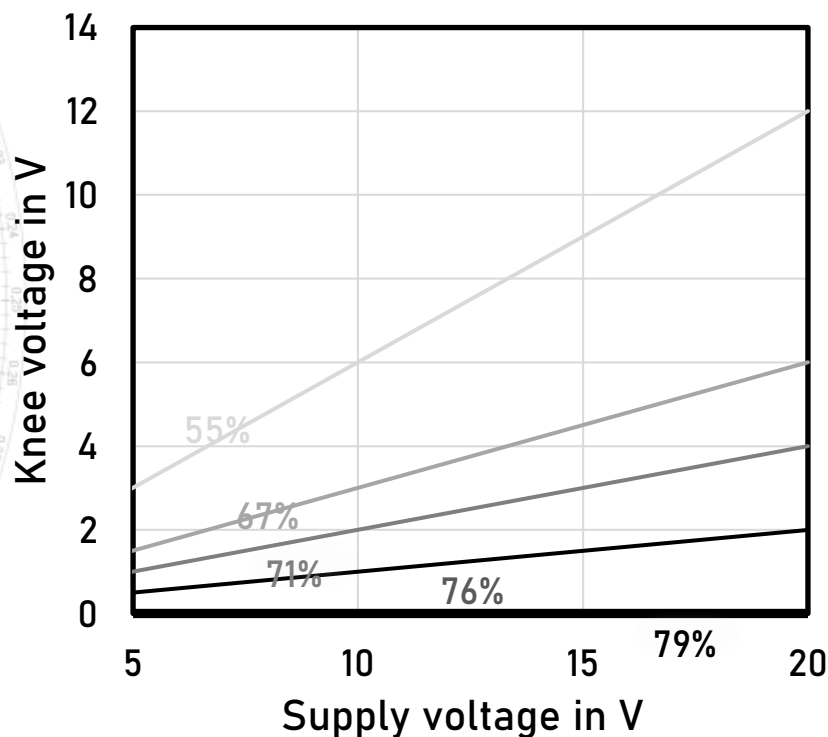
- In GaN HEMTs, electrons get trapped by high electric fields, that increases the size of the linear region (or knee region)
- This gives us less voltage to work with and thus lower power and efficiency
- This effect is invisible when doing normal DCIV measurements



Advanced RF IV Waveform Engineering Tool for use in device technology optimization: *RF Pulsed Fully Active Harmonic Load Pull with Synchronized 3eV Laser*


Getting the Efficiency up

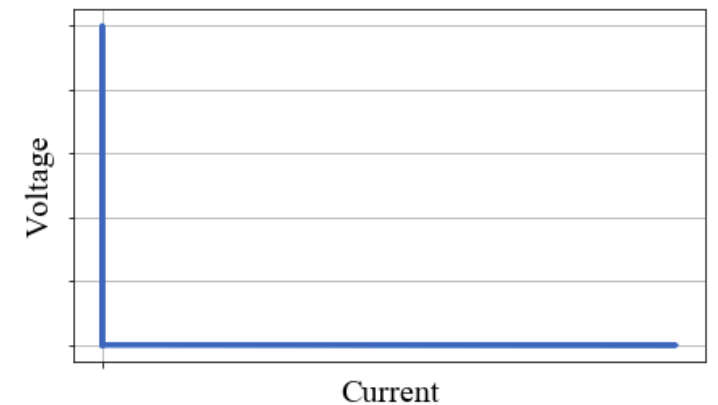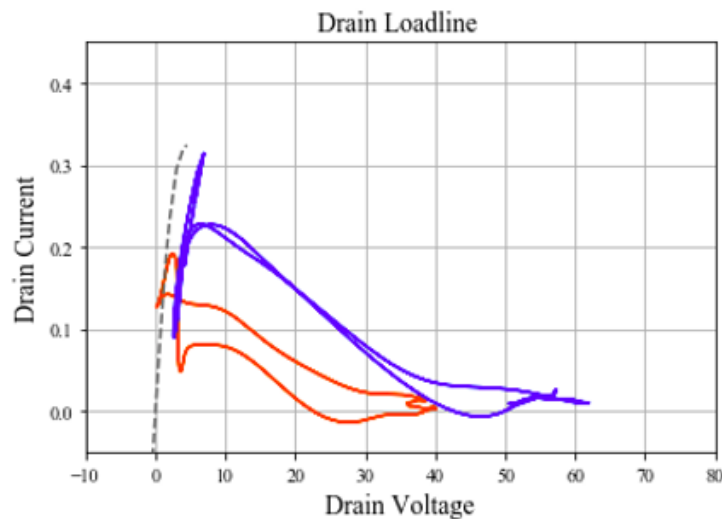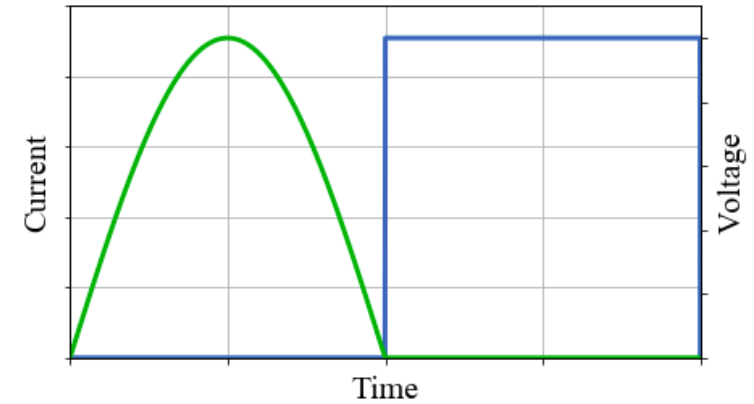- Class F, class E, class D, class X (really!)
- Reducing voltage current overlap
- In load lines: No voltage if current non-zero and vice versa
- Realistically, 70% - 85% are achievable (depending on frequency)






Keeping Efficiency high

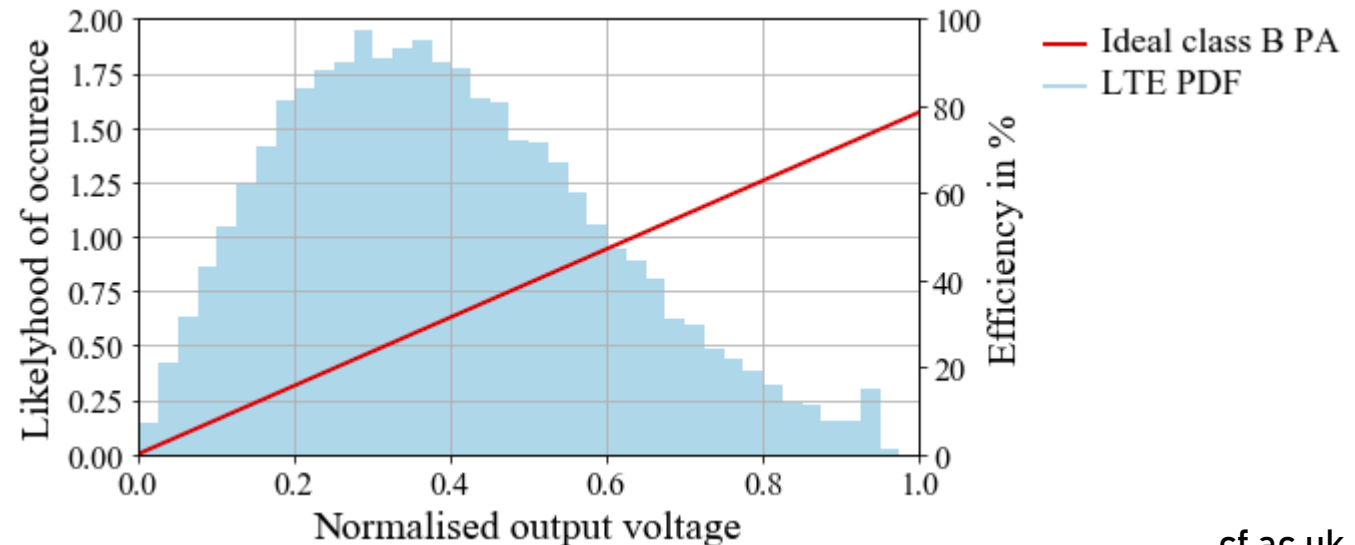- Most modulation schemes operate PA in back-off
- Operate at relatively low output power most of the time but need to be able to provide high powers at the same time
- Unfortunately, PA is very inefficient there




Keeping Efficiency high

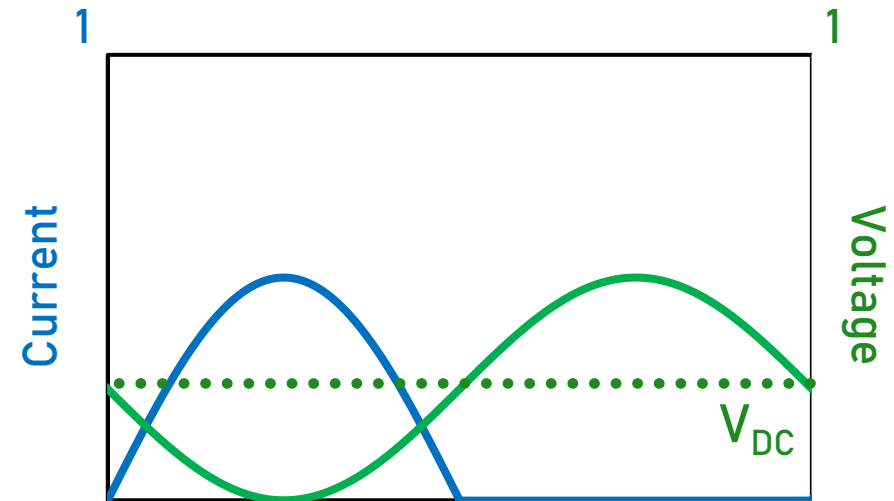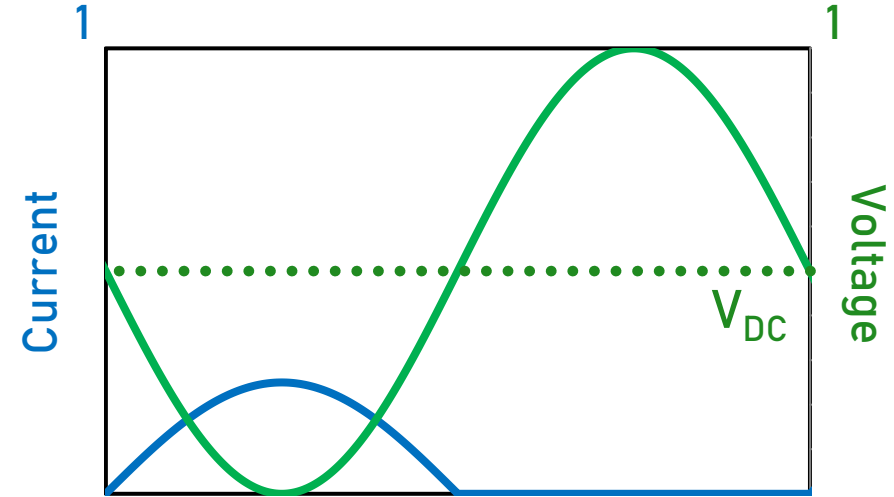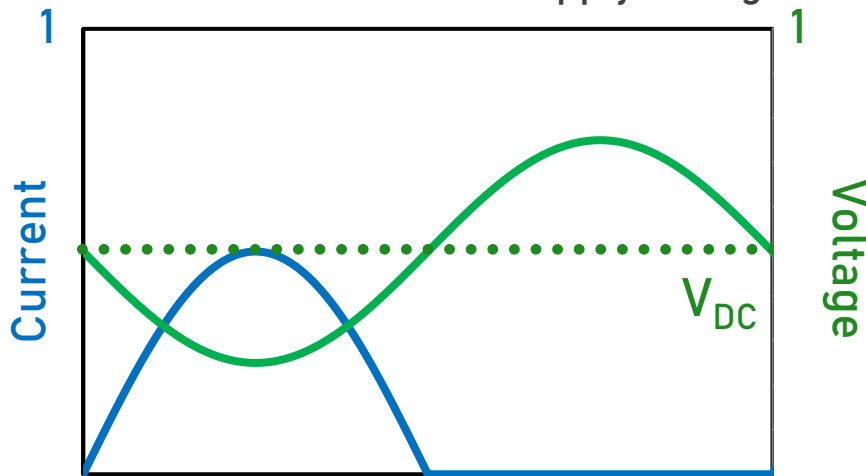- Inefficiency due to voltage not reaching knee
- Can be fixed by introducing additional transistors
 - To modulate the RF load impedance
 - To modulate the supply voltages




Supply Modulation

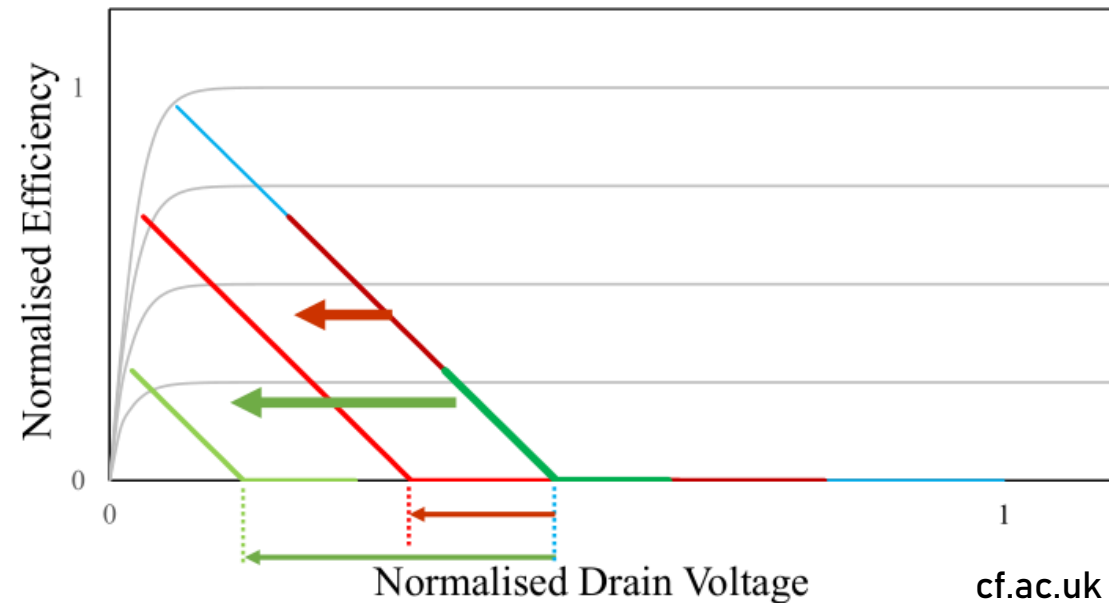- Constant RF load impedance
- Change supply voltage with modulation
- Keep voltage swing but move minimum closer to knee region
- Requires the supply voltage to change
 - Easy for slow signals
 - Very challenging for modulation frequencies in modern communication systems




Load Modulation

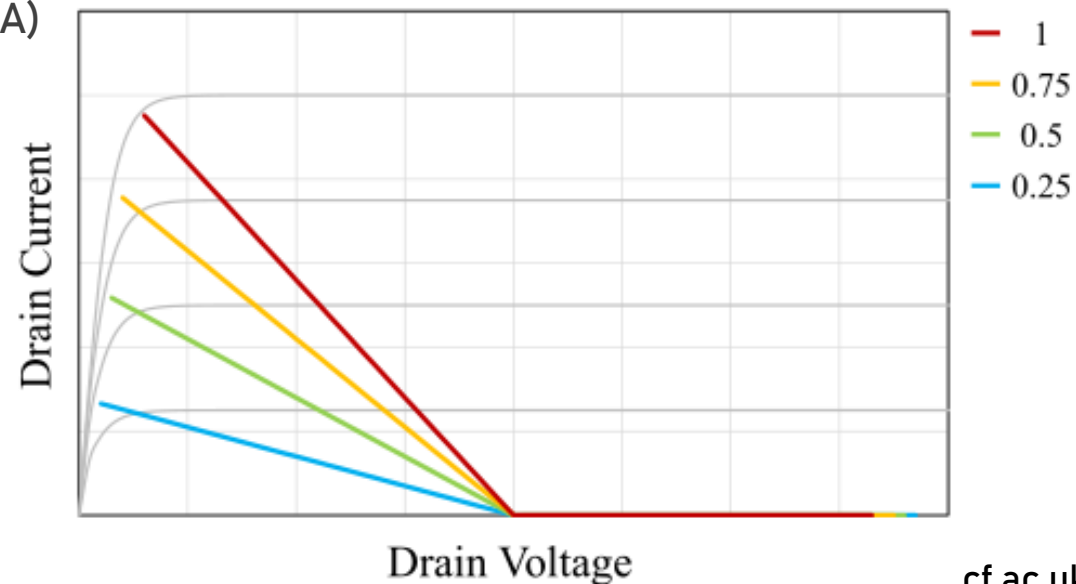- Constant supply voltage
- Change in load impedance reduces losses
- Keeps PA efficient over large power ranges
- Different ways to realise it
 - Use two amplifiers (Doherty, outphasing)
 - A balanced PA and a control signal (LMBA)
 - Adjustable matching network (passive load modulation)




Rectifiers

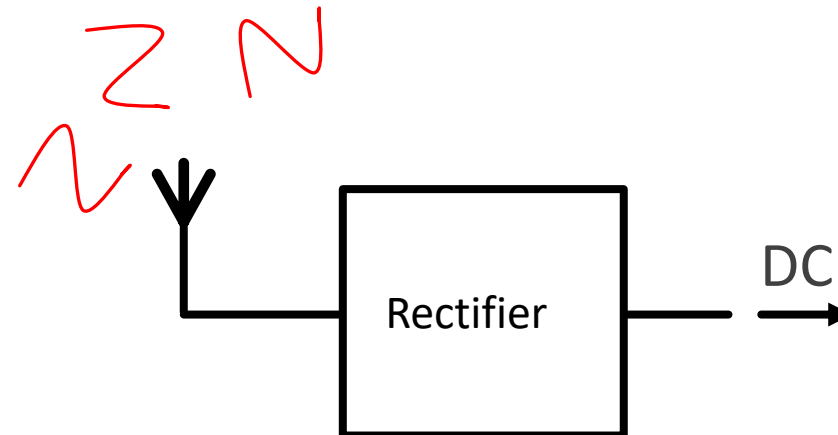- Convert RF power to DC power
- Ubiquitous RF power -> Many applications
 - Energy harvesting
 - Wireless power transmission
 - RF DC/DC converters





Rectifiers

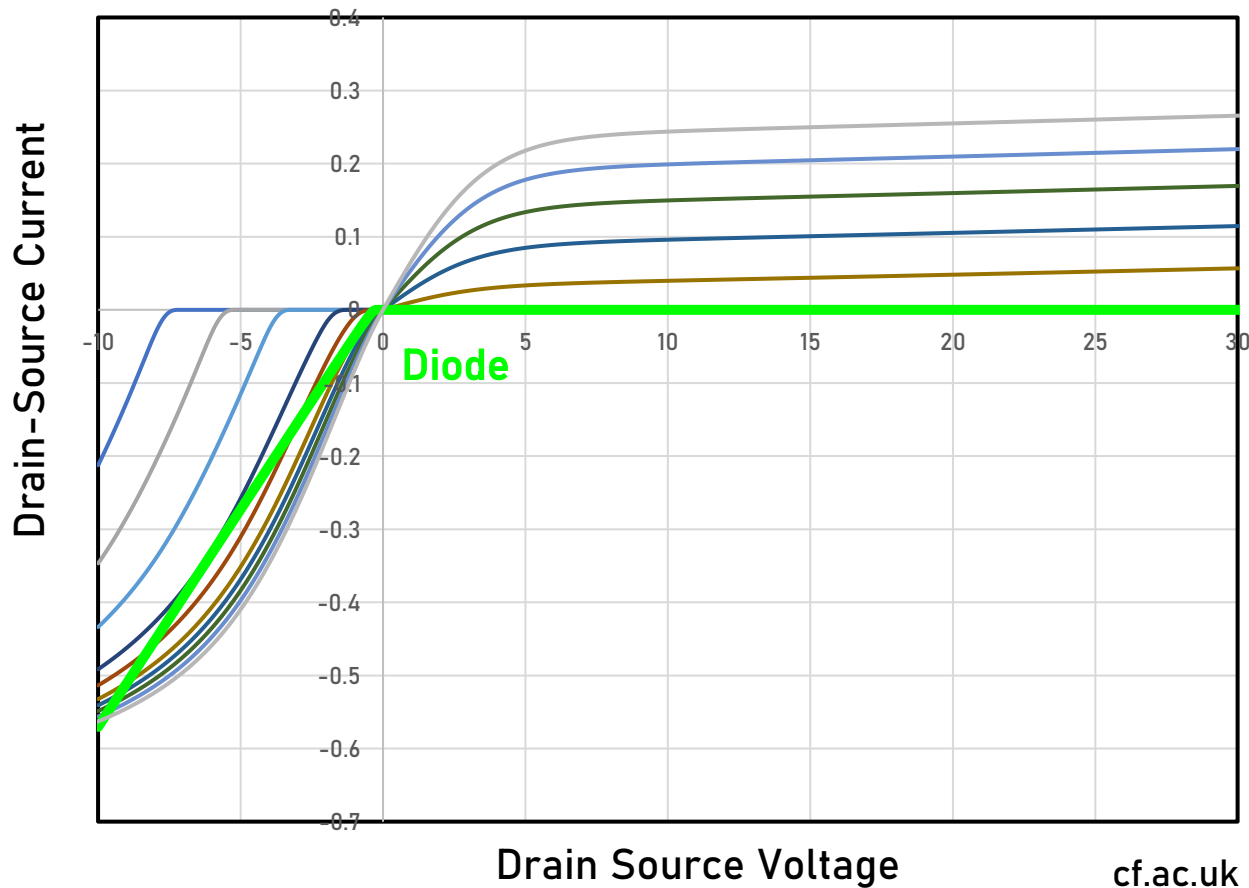- ▶ Can use diodes or transistors (depending on technology!)
- ▶ Transistors allow higher efficiencies at RF, over 90% RF \rightarrow DC efficiency but they need gate signal (depending on technology!)
- ▶ IV curves now extend to negative drain source voltages



Rectifiers

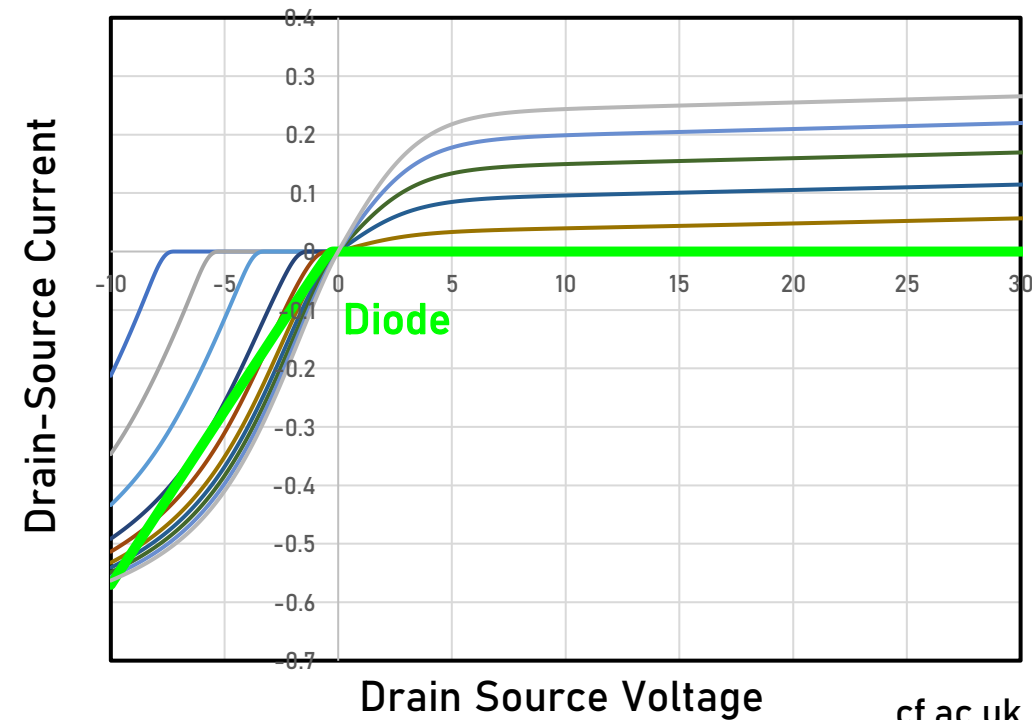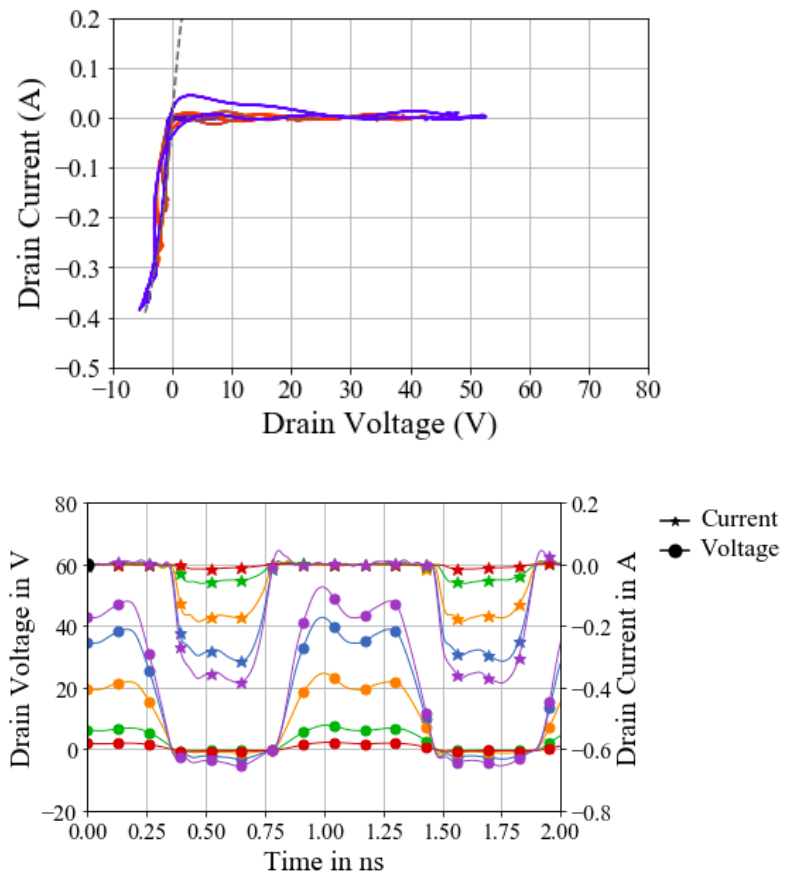- We have load-lines in rectifiers, both diode and transistor based ones!




Conclusion

- Loadlines are a useful tool to visualise voltage and currents of transistors
- Can be used in a wide range of applications
- Using simple measurements, a lot of information about a transistor can be obtained
- This can be used to design PAs or form the basis for the basis for

Thanks for listening!

References

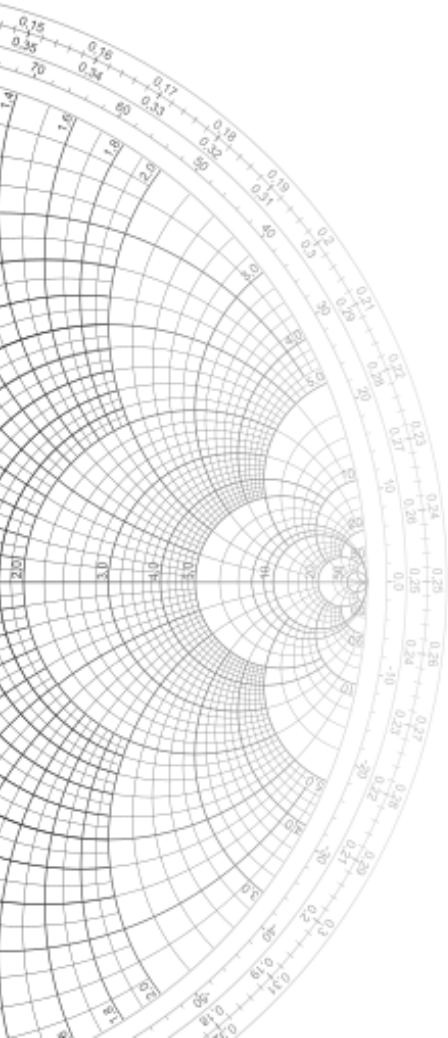- 
- [1] E. McCune, Dynamic Power Supply Transmitters. Cambridge University Press, 2015, Cambridge Books Online.
 - [2] Z. Yusoff, M. Akmal, V. Carrubba, J. Lees, J. Benedikt, P. J. Tasker, and S. C. Cripps, “The benefit of GaN characteristics over LDMOS for linearity improvement using drain modulation in power amplifier system,” in 2011 Workshop on Integrated Nonlinear Microwave and Millimetre-Wave Circuits, Apr. 2011, pp. 1–4.
 - [3] M. Mercanti, A. Cidronali, S. Maurri, and G. Manes, “HEMT GaAs/GaN power amplifiers architecture with discrete dynamic voltage bias control in envelope tracking RF transmitter for W-CDMA signals,” in 2011 IEEE Topical Conference on Power Amplifiers for Wireless and Radio Applications, 2011, pp. 9–12.
 - [4] M. Olavsbråten, D. Gecan, M. R. Duffy, G. Lasser, and Z. Popovic, “Efficiency enhancement and linearization of GaN PAs using reduced-bandwidth supply modulation,” in 2017 47th European Microwave Conference (EuMC), 2017, pp. 456–459.
 - [5] Z. A. Mokhti, P. J. Tasker, and J. Lees, “Analyzing the improvement in efficiency through the integration of class-F power amplifiers compared to class-AB in an envelope tracking architecture,” in 2014 26th International Teletraffic Congress (ITC), Sep. 2014, pp. 1–4.
 - [6] Nitronex AN-011: Substrates for GaN RF Devices
 - [7] NXP, MRFE6VS25LR5 Datasheet, 5th ed., Freescale, 2012.
 - [8] MaCOM, Ed., NPT1012 Datasheet, 2013.
 - [9] Qorvo, TGF2080 Datasheet, 2013.